

Circuits & Schematics

August 28, 2018

Reminders

Bring something to hack on Thursday

You should have a class buddy

Circuits





Common Components | Voltage | Current | Resistance

Ohms Law | Watt's Law | Series and Parallel Circuits

Voltage Divider | Pull-up and Pull-down circuits

Electrical circuits are networks of electrical elements that contain a closed loop which allows electrons to flow through the elements.

Examples of Electrical Components

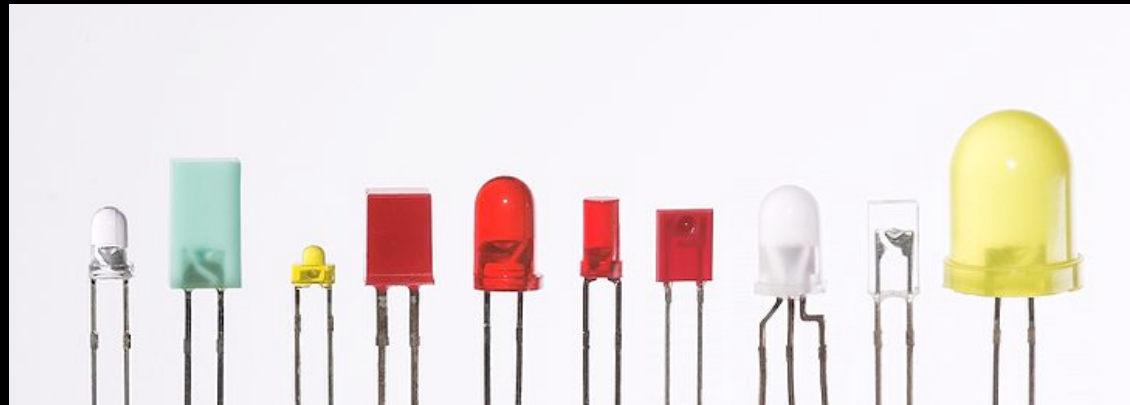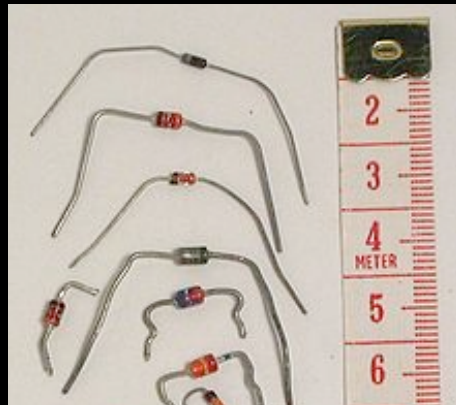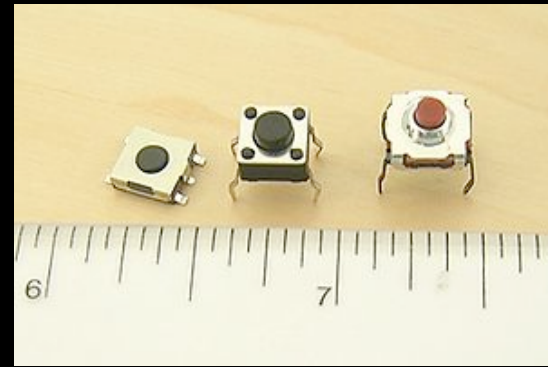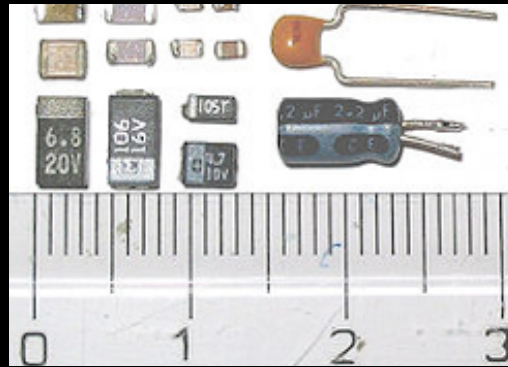

images from Wikipedia

Current (measured in Amperes or Amps) is the quantity of electrons passing through a point in a circuit. **I**

Voltage (measured in Volts) is the potential difference in electrical charge between two points in a circuit. **V**

Resistance (measured in Ohms - Ω) is the capacity of a circuit element to impede the flow of electrons in an electrical circuit. **R**

Current flows with almost no resistance in metal, and so things that are connected by direct metal-on-metal contact share the same voltage.

Sketching in Hardware



image from <https://learn.sparkfun.com/tutorials/how-to-use-a-breadboard>

originally from <http://www.instructables.com/id/Use-a-real-Bread-Board-for-prototyping-your-circui/>



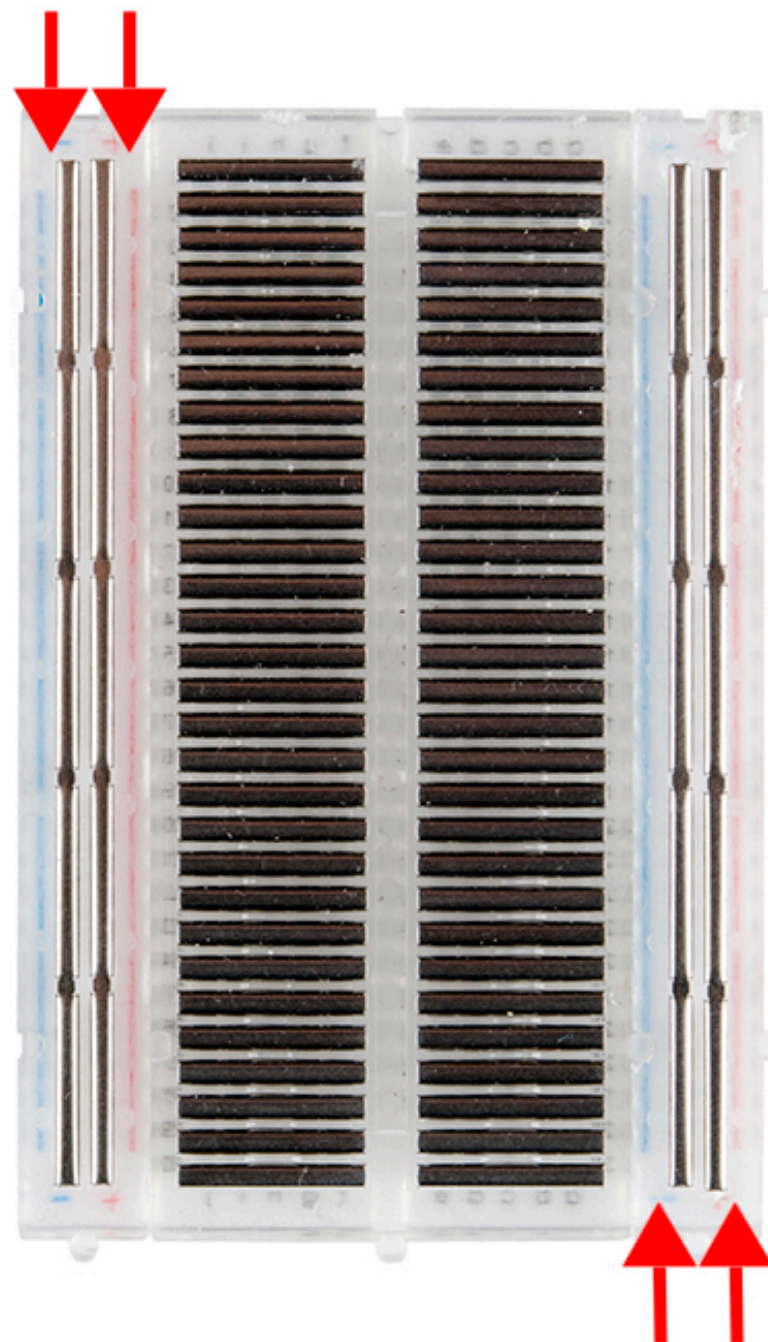


image from <https://learn.sparkfun.com/tutorials/how-to-use-a-breadboard>

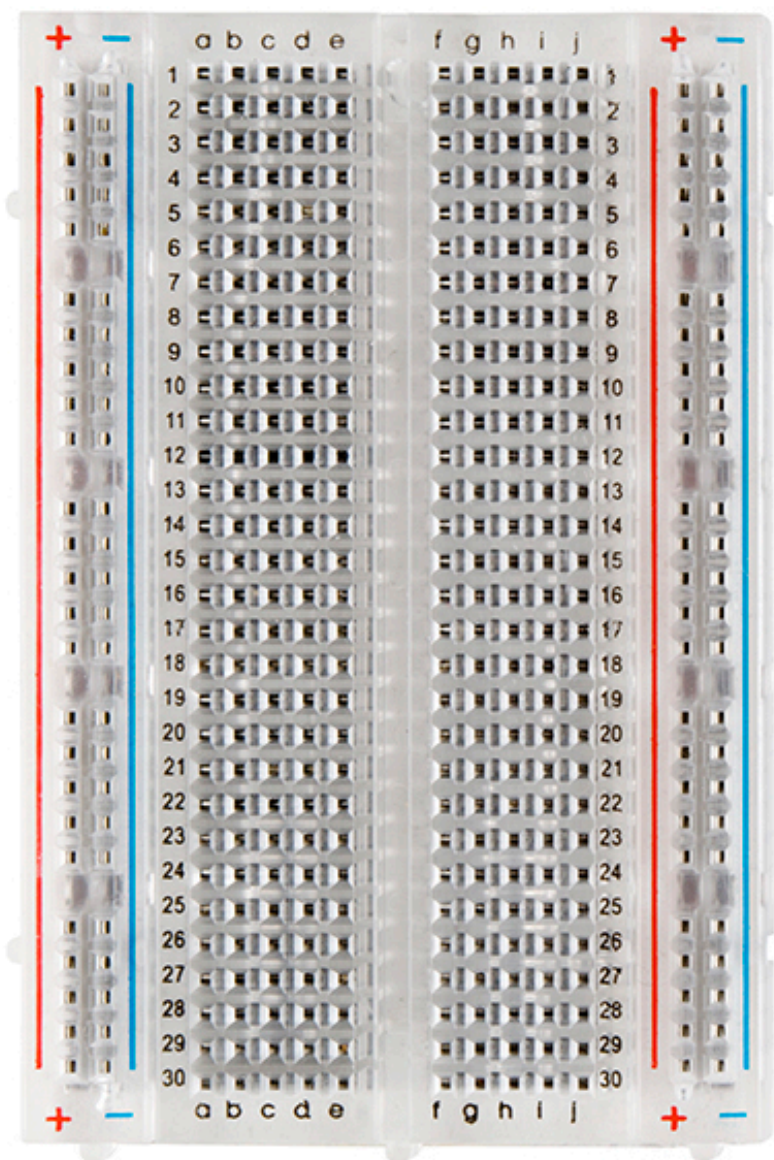


image from <https://learn.sparkfun.com/tutorials/how-to-use-a-breadboard>

SOLDER-LESS BREAD BOARD

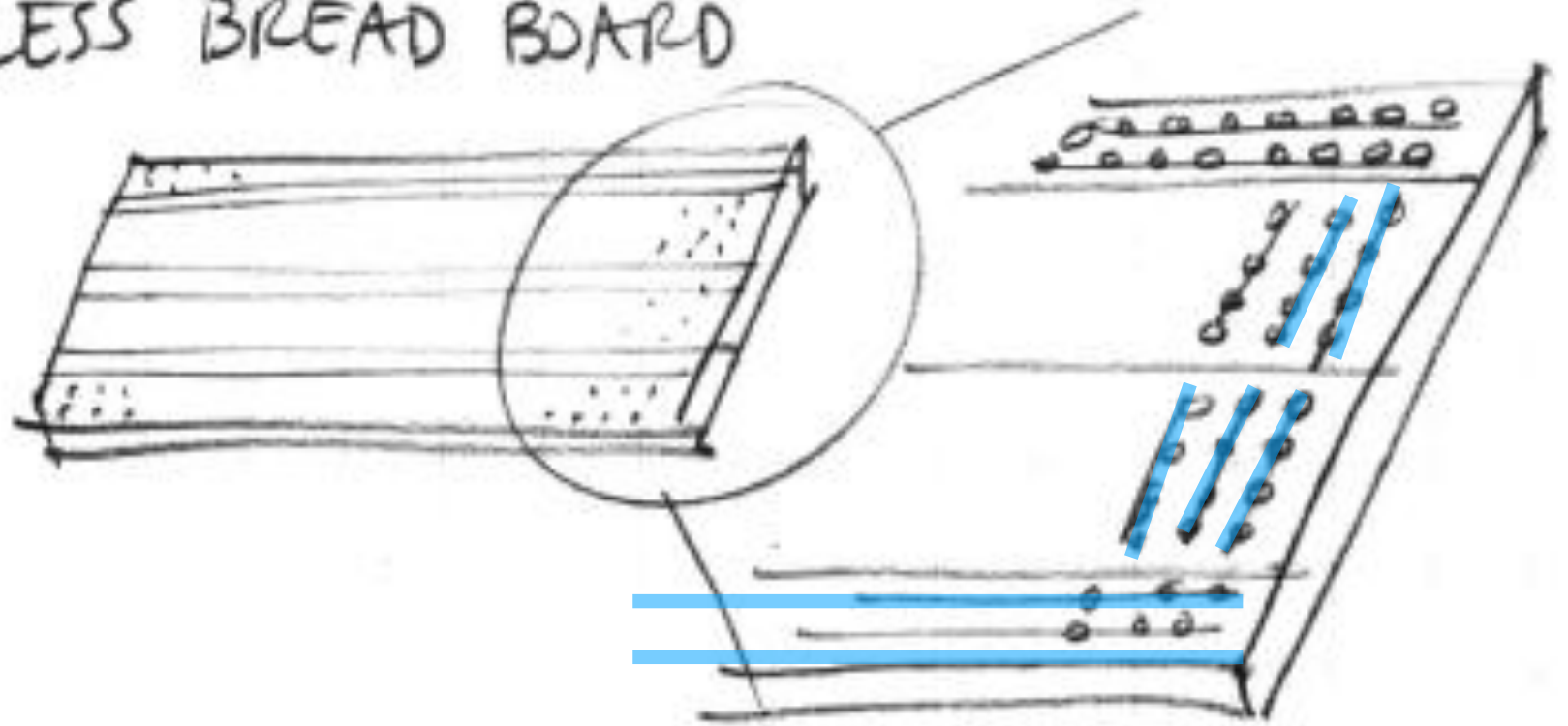


sketch by Bill Verplank

SOLDER-LESS BREAD BOARD

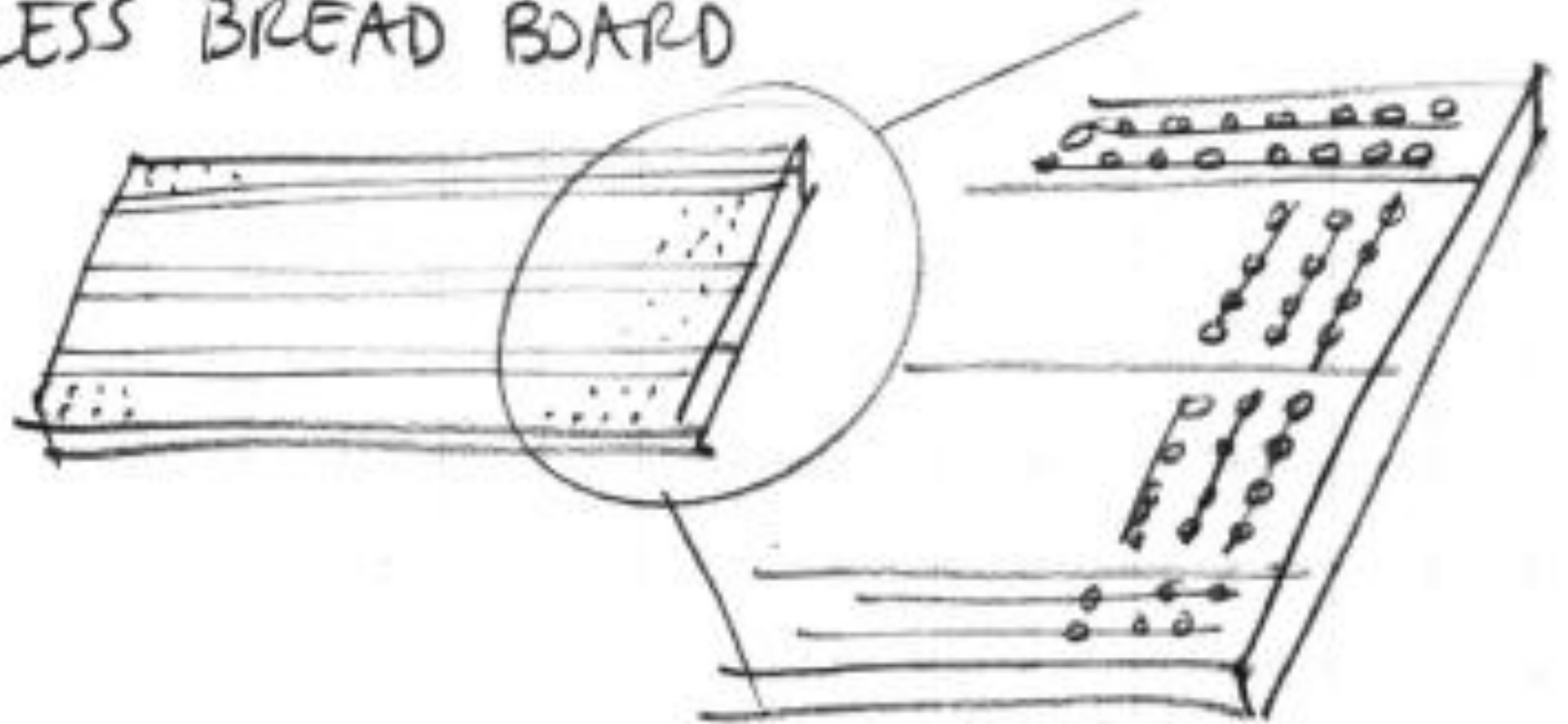

sketch by Bill Verplank

Pushbutton LED circuit

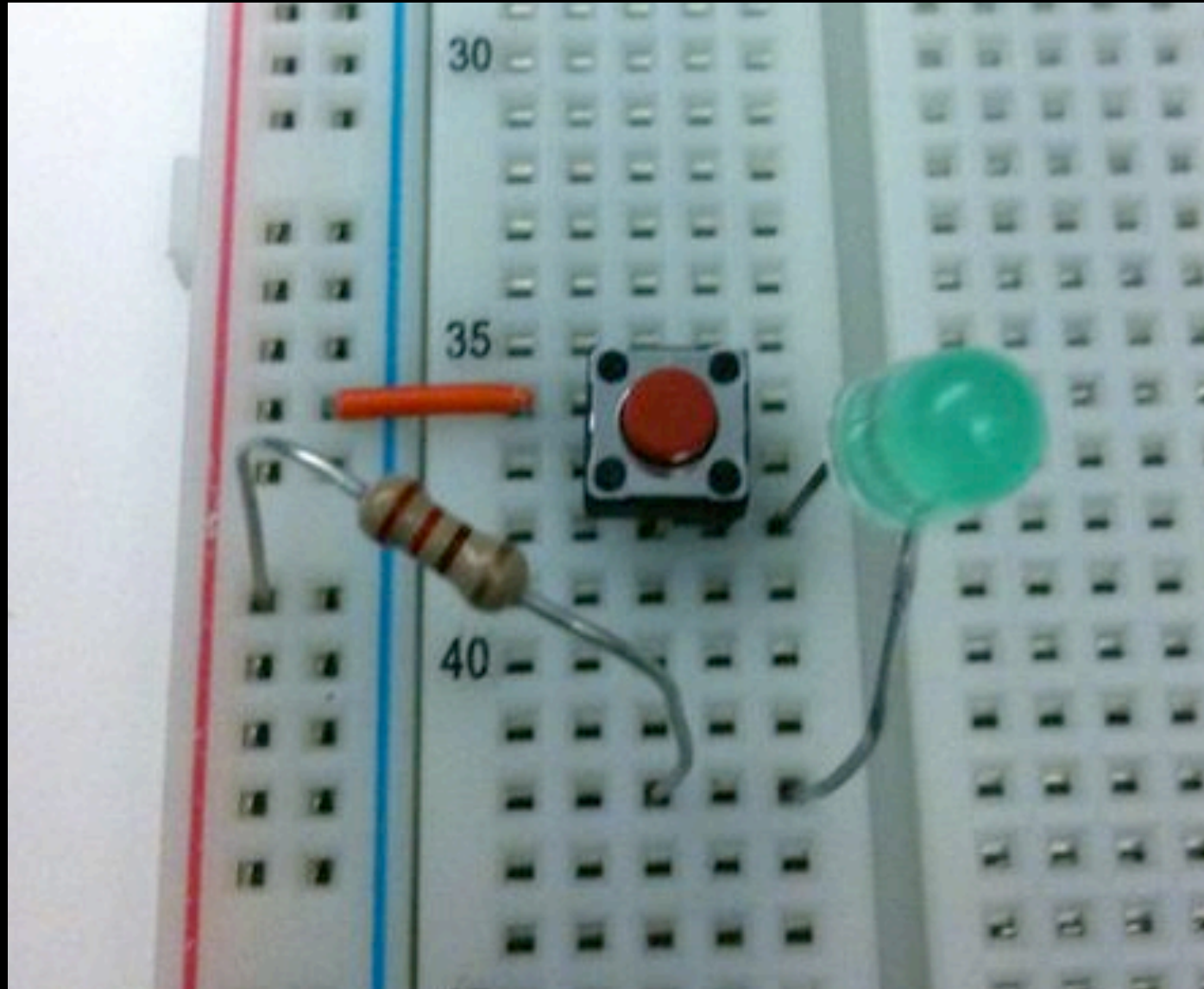

Pushbutton LED circuit breadboard drawing


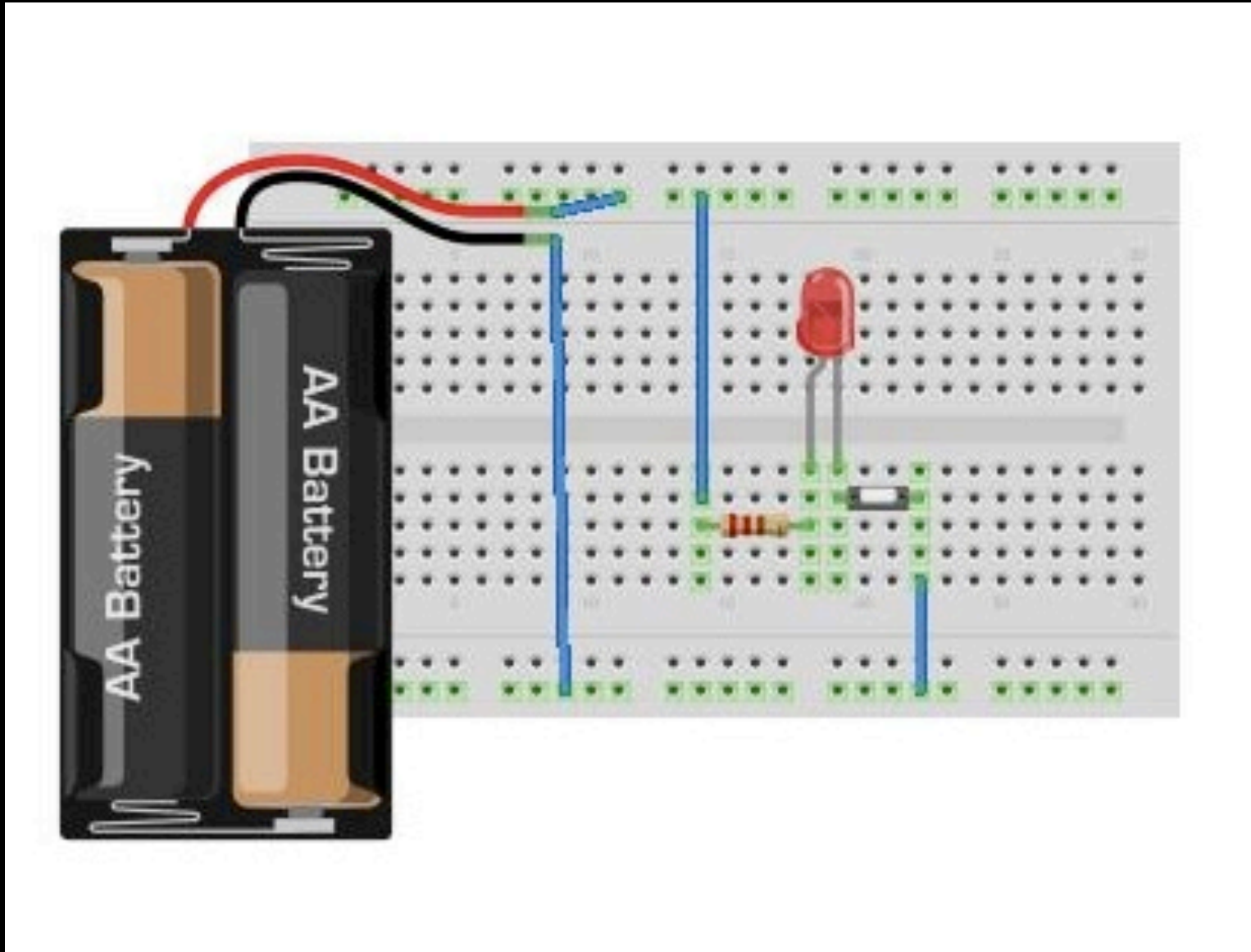
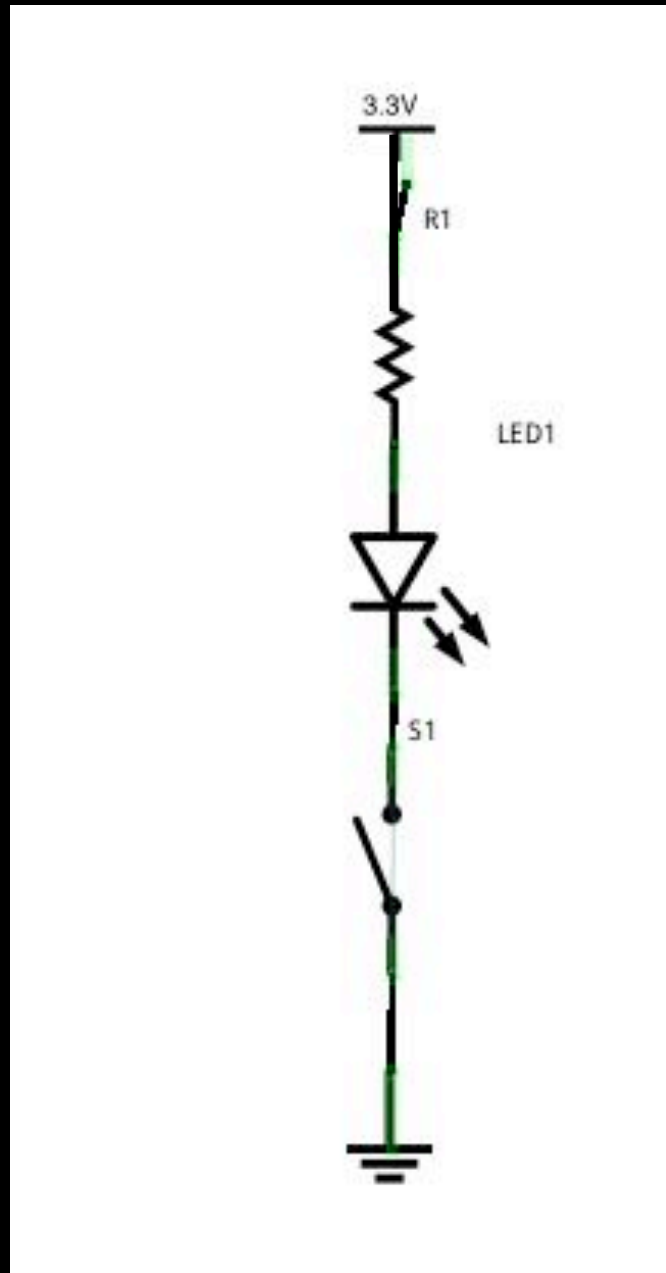


diagram made in Fritzing


Pushbutton LED circuit schematic

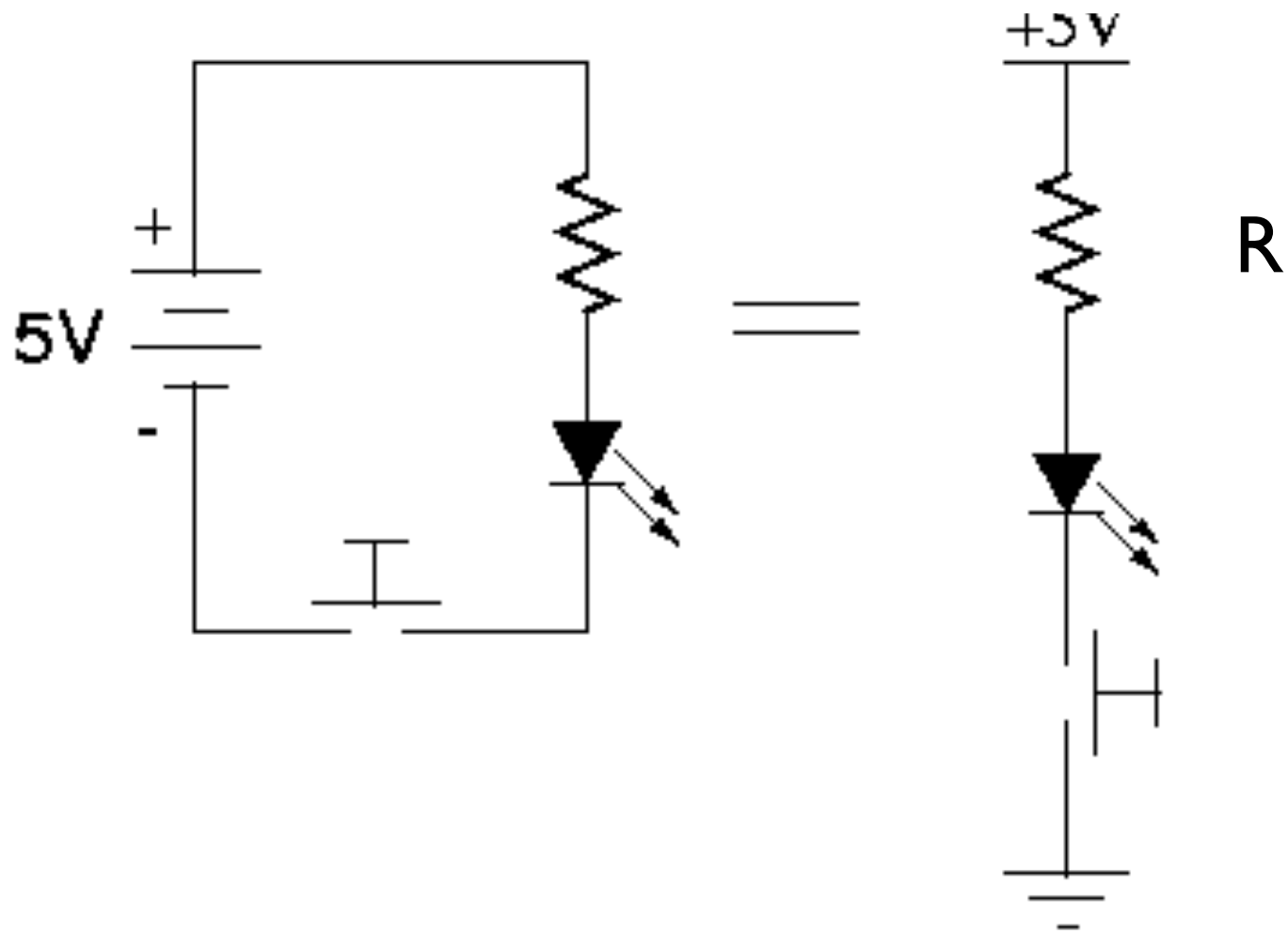

Power in the Pushbutton LED circuit

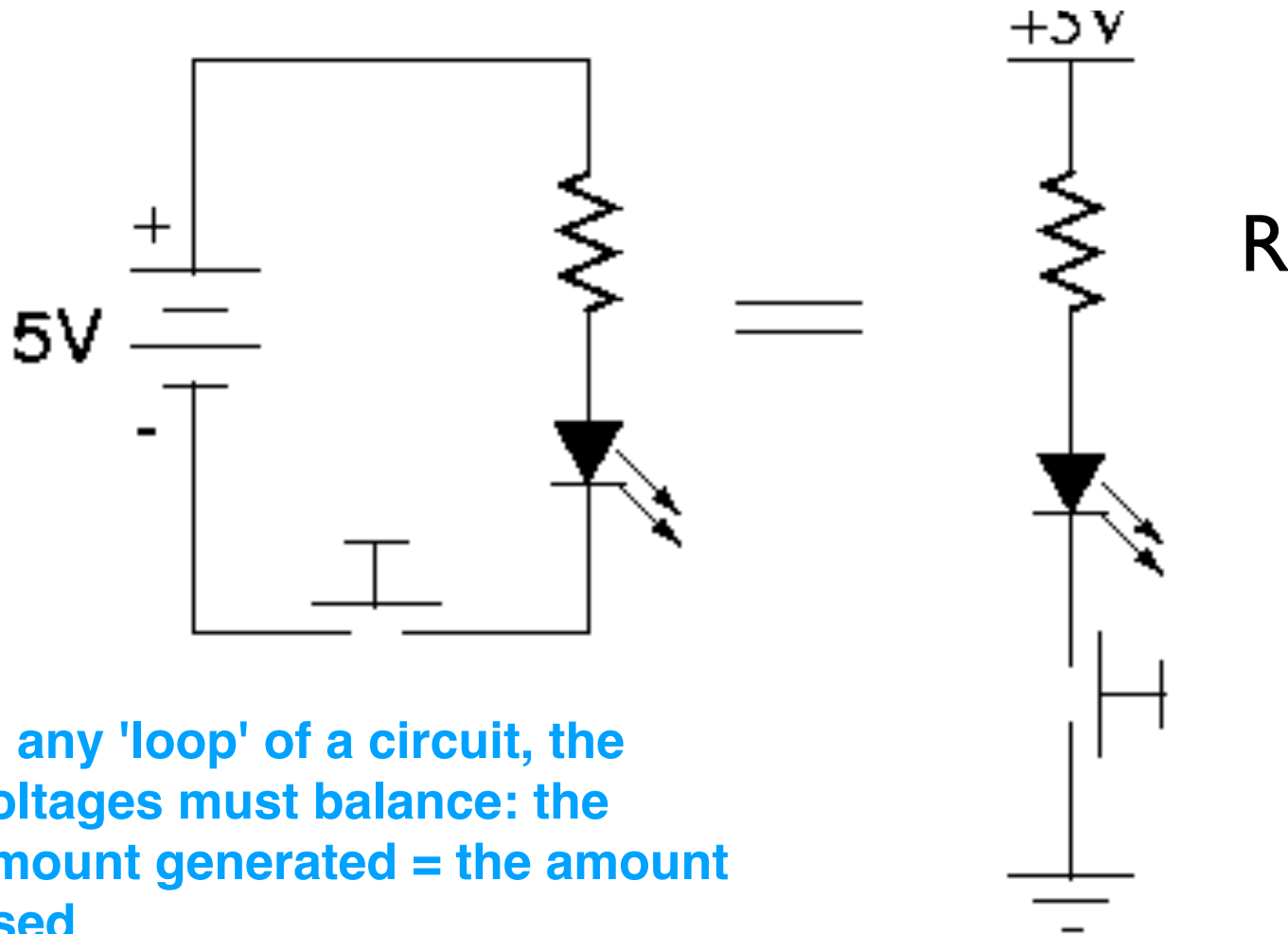
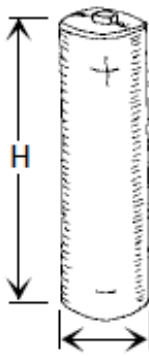
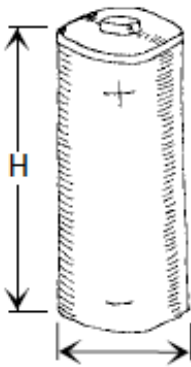
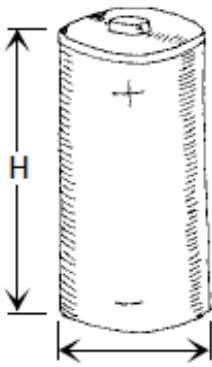
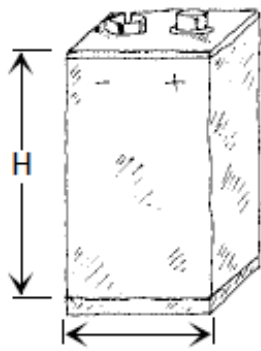


KIRCHOFF'S LAW in the Pushbutton LED circuit



In any 'loop' of a circuit, the voltages must balance: the amount generated = the amount used

Common Alkaline and Carbon Zinc Cells

1.5V "AAA"		1.5V "AA"		1.5V "C"		1.5V "D"		"9V"		
										
D	H	D	H	D	H	D	H	W	L	H
0.41"	1.75"	0.56"	1.97"	1.02"	1.97"	1.32"	2.39"	1.03"	0.65"	1.91"
$\left(\frac{13}{32}\right)$	$\left(1\frac{31}{32}\right)$	$\left(\frac{9}{16}\right)$	$\left(1\frac{31}{32}\right)$	$\left(1\frac{1}{64}\right)$	$\left(1\frac{31}{32}\right)$	$\left(\frac{11}{32}\right)$	$\left(2\frac{27}{64}\right)$	$\left(\frac{13}{32}\right)$	$\left(\frac{11}{16}\right)$	$\left(1\frac{15}{16}\right)$

Lithium



Voltage:
 1.55 to 6V
 Diameter:
 0.460 to 0.965"
 Thicknesses:
 0.079" to 0.990"
 mAh:
 60 to 250 mAh
 Label:
 Given in I.E.C.
 number (e.g.,
 CRXXX or BRXXX)

Zinc air



Voltage:
 1.15 to 1.4V
 mAh:
 70 to 600 mAh
 Labels:
 ZAXXX

Mercury




Voltage:
 1.35 to 5.6V
 Diameter:
 0.5 to 0.695"
 Thicknesses:
 0.135" to 0.845"
 mAh:
 80 to 1000 mAh

Silver oxide




Voltage:
 1.55V
 Diameter:
 0.267 to 0.610"
 Thicknesses:
 0.081" to 0.210"
 mAh:
 15 to 250 mAh
 Label:
 Given in I.E.C.
 number (e.g., SRXX)

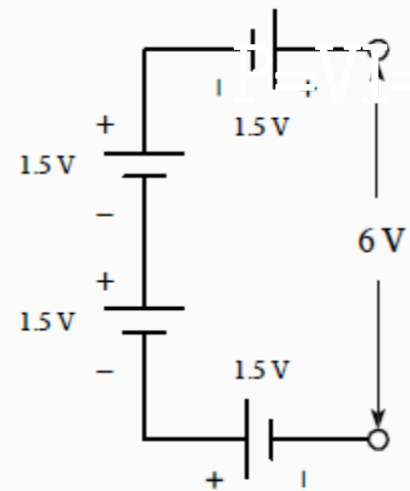
Power can come from supplies or batteries.



Increasing the voltage

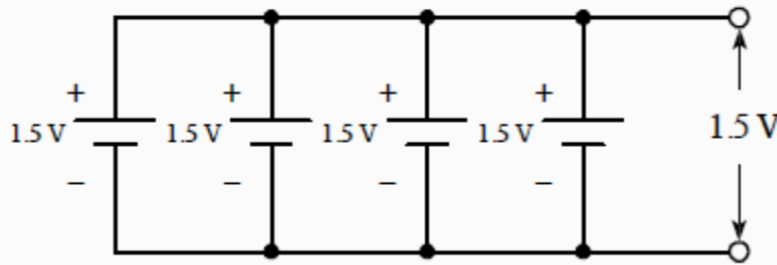

Increasing the capacity

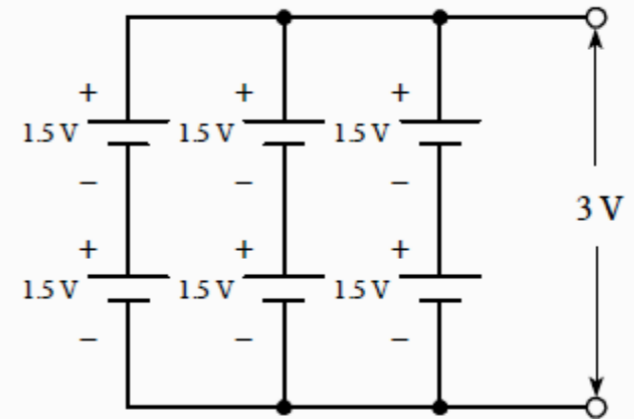

Increasing both voltage and capacity

Power Supply



5V DC to DC Step Up - 1xAA




ENERGIZER CR2032

Lithium Coin



Industry Standard Dimensions

mm (inches)

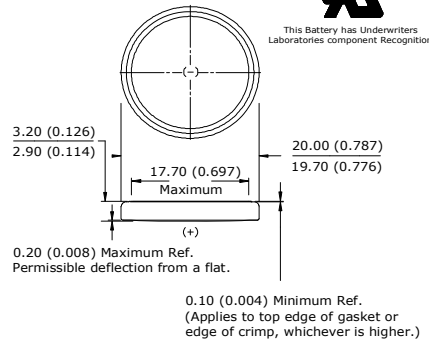

Classification:

Chemical System:

Designation:

Nominal Voltage:

Typical Capacity:

Typical Weight:

Typical Volume:

Typical IR:

Max Rev Charge:

Energy Density:

Typical Li Content:

UL Listed:

Shipping:

Specifications

"Lithium Coin"

Lithium / Manganese Dioxide (Li/MnO₂)

ANSI / NEDA-5004LC, IEC-CR2032

3.0 Volts

240 mAh (to 2.0 volts)

(Rated at 15K ohms at 21°C)

3.0 grams (0.10 oz.)

1.0 cubic centimeters (0.06 cubic inch)

10,000 - 40,000 mΩ

1 microampere

198 milliwatt hr/g, 653 milliwatt hr/cc

0.109 grams (0.0038 oz.)

MH12454

For complete details, please reference:

Global (except US): Special Provision A45 of the International

Air Transport Association Dangerous

Goods Regulations

United States: 49 CFR 173.185


Safety:




(1) KEEP OUT OF REACH OF CHILDREN. Swallowing may lead to serious injury or death in as little as 2 hours due to chemical burns and potential perforation of the esophagus. **Immediately see doctor; have doctor phone (202) 625-3333.**

(2) Battery compartment design. To prevent children from removing batteries, battery compartments should be designed with one of the following methods: a) a tool such as screwdriver or coin is required to open battery compartment or b) the battery compartment door/cover requires the application of a minimum of two independent and simultaneous movements of the securing mechanism to open by hand. Screws should remain captive with the battery door or cover.

Continuous Discharge Characteristics

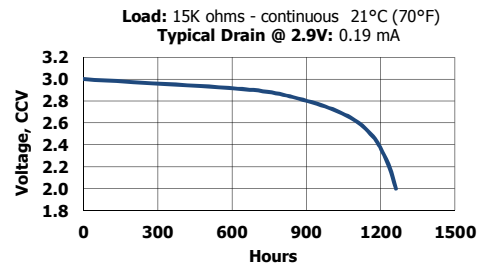

Cross Section

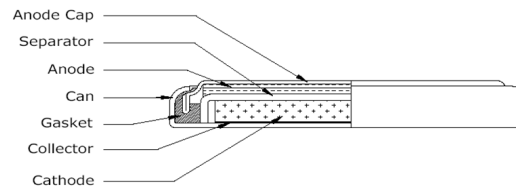

Simulated Application test

Typical Performance at 21°C (70°F)


Schedule:	Typical Drains: at 2.9V (mA)	Load (ohms)	Cutoff 2.0V (hours)
Continuous	0.043	68,000	721

Important Notice


This datasheet contains typical information specific to products manufactured at the time of its publication.

©Energizer Holdings, Inc. - Contents herein do not constitute a warranty.

Input in the Pushbutton LED circuit

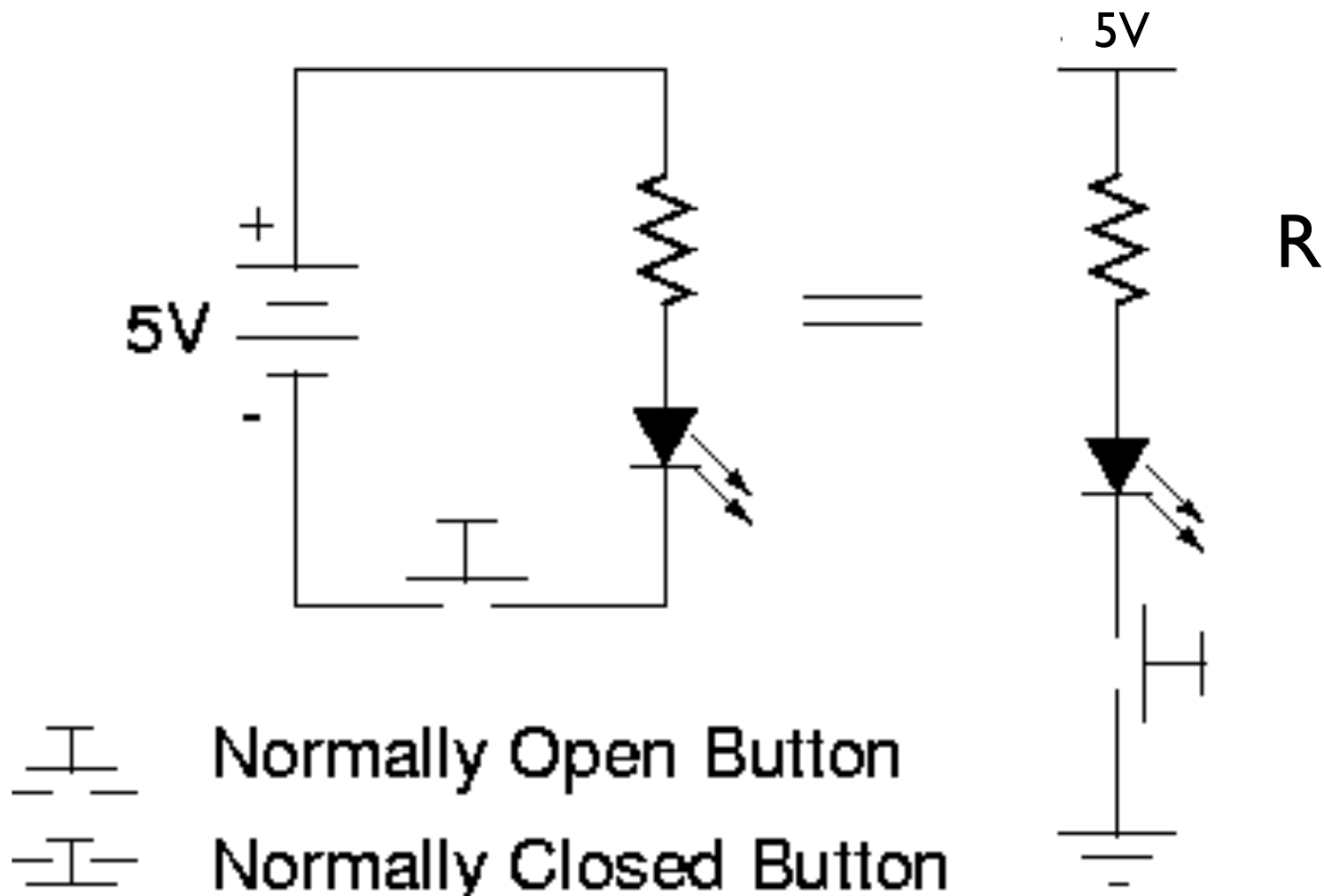

Switches/Buttons

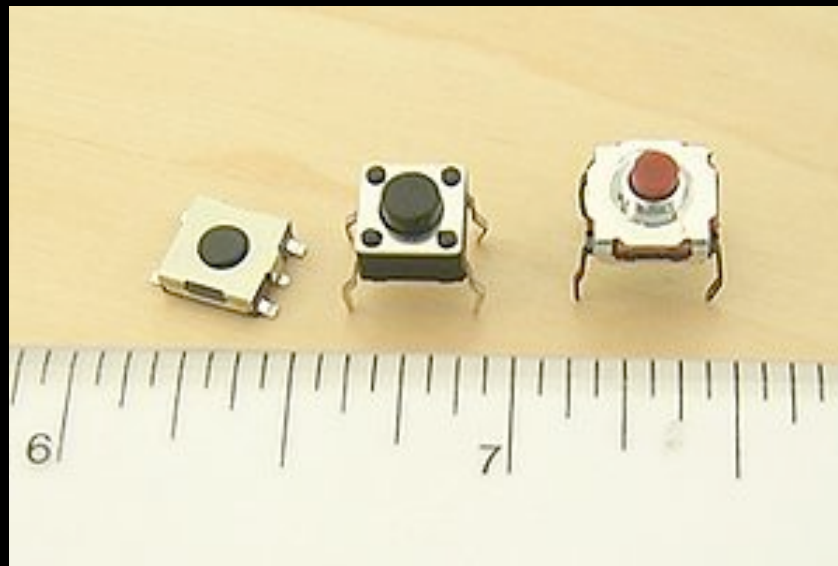


images from Wikipedia


Switches/Buttons



Output in the Pushbutton LED circuit

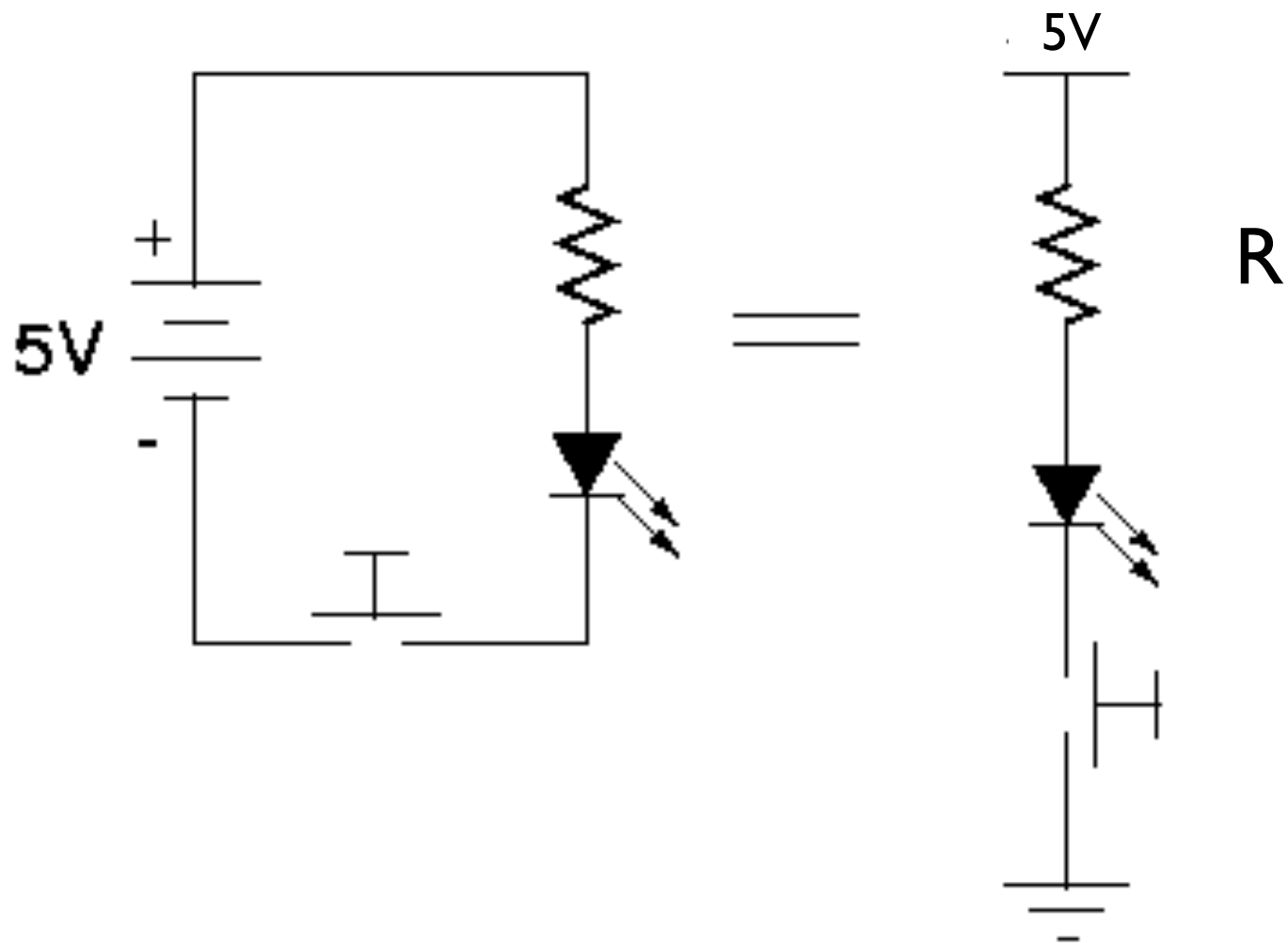

LEDs

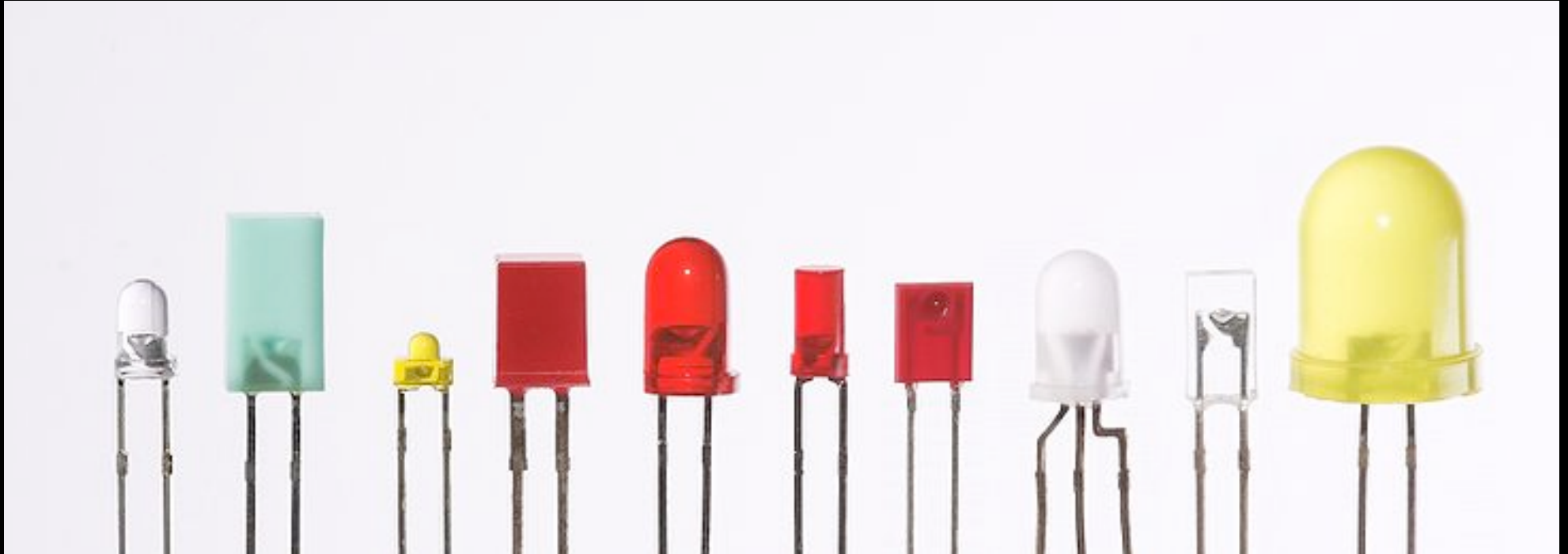

images from Wikipedia

LED datasheet

<https://learn.adafruit.com/all-about-leds/the-led-datasheet>

Kingbright

T-1 3/4 (5mm) SOLID STATE LAMP

Part Number: WP7113SRD/D

Super Bright Red


Features

- LOW POWER CONSUMPTION.
- POPULAR T-1 3/4 DIAMETER PACKAGE.
- GENERAL PURPOSE LEADS.
- RELIABLE AND RUGGED.
- LONG LIFE - SOLID STATE RELIABILITY.
- AVAILABLE ON TAPE AND REEL.
- RoHS COMPLIANT.

Description

The Super Bright Red source color devices are made with Gallium Aluminum Arsenide Red Light Emitting Diode.

Package Dimensions

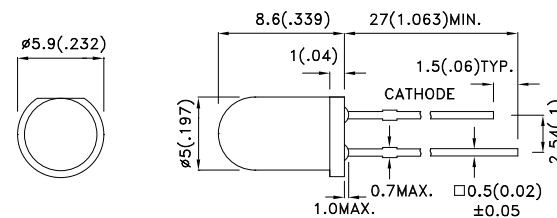

Notes:

1. All dimensions are in millimeters (inches).
2. Tolerance is $\pm 0.25(0.01")$ unless otherwise noted.
3. Lead spacing is measured where the leads emerge from the package.
4. Specifications are subject to change without notice.




SPEC NO: DSAF2433
APPROVED: WYNEC

REV NO: V.2
CHECKED: Allen Liu




DATE: MAY/11/2007
DRAWN: Y.L.LI

PAGE: 1 OF 6
ERP: 1101005271-02


Inside LEDs

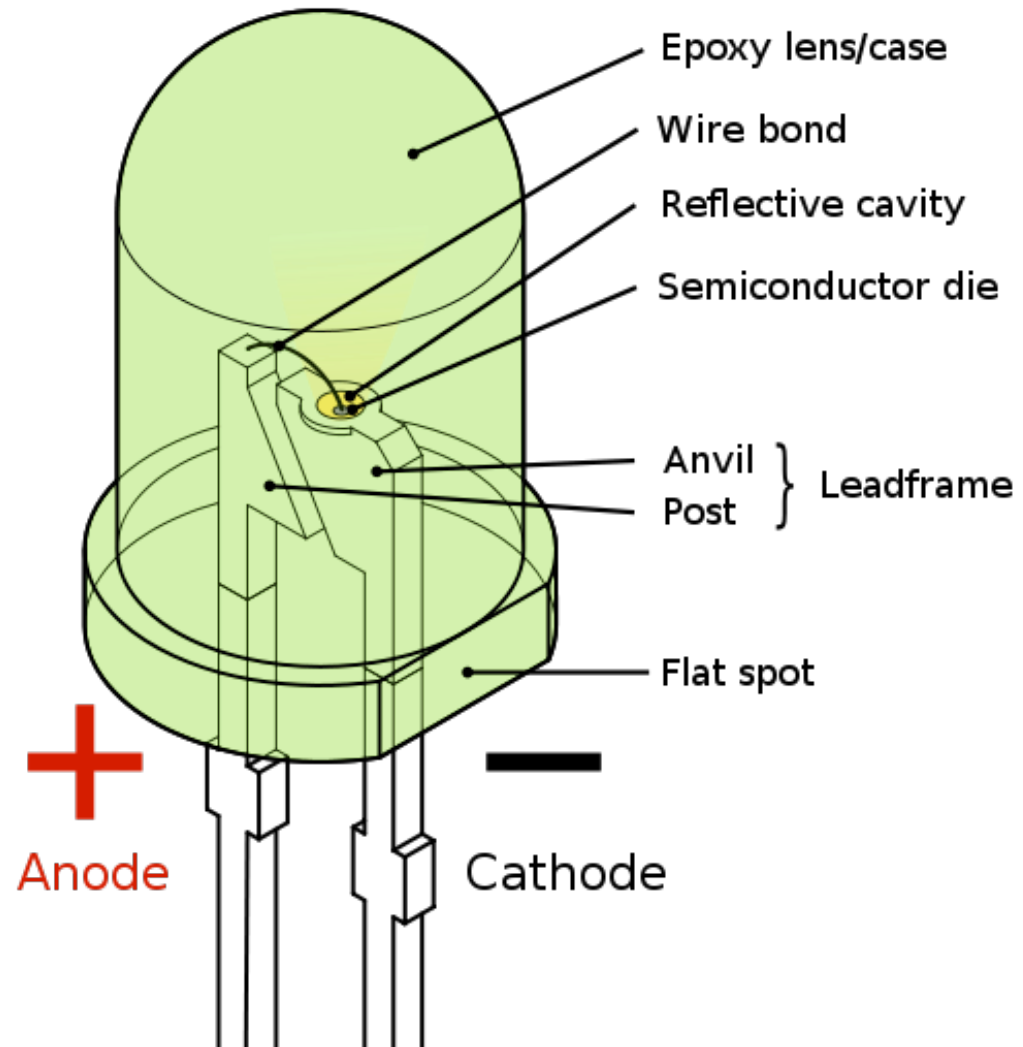

RGB LEDs

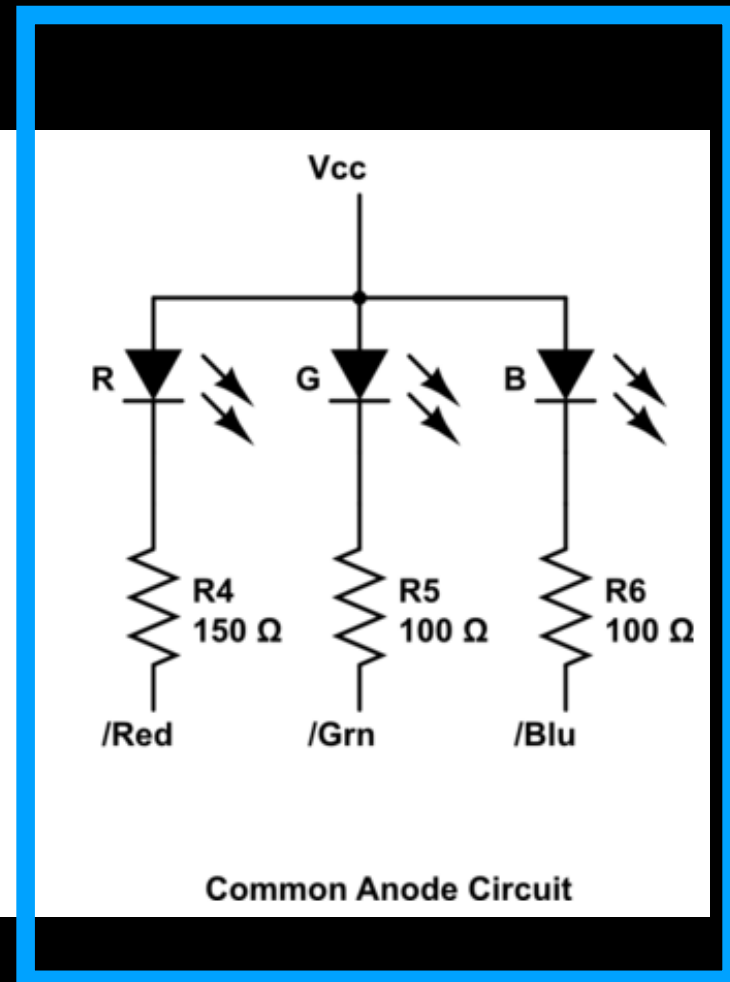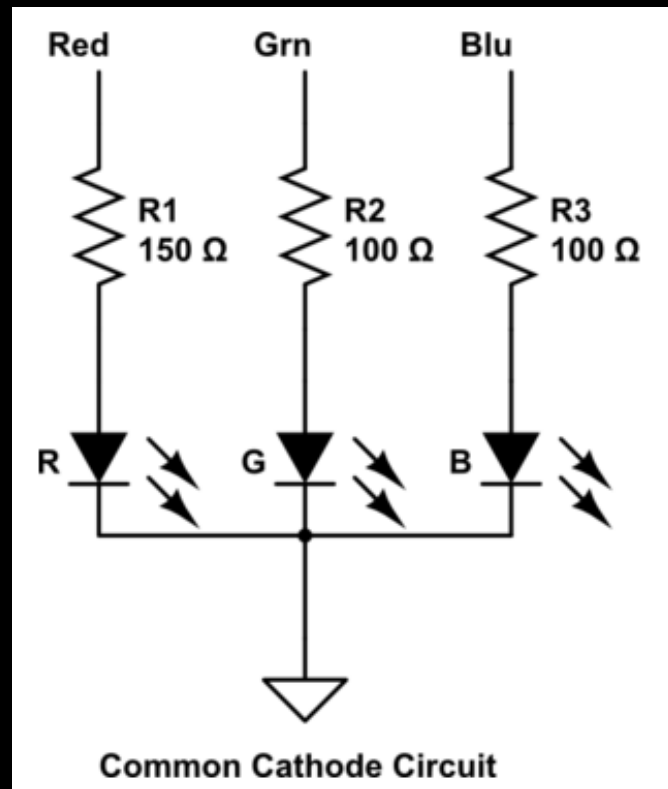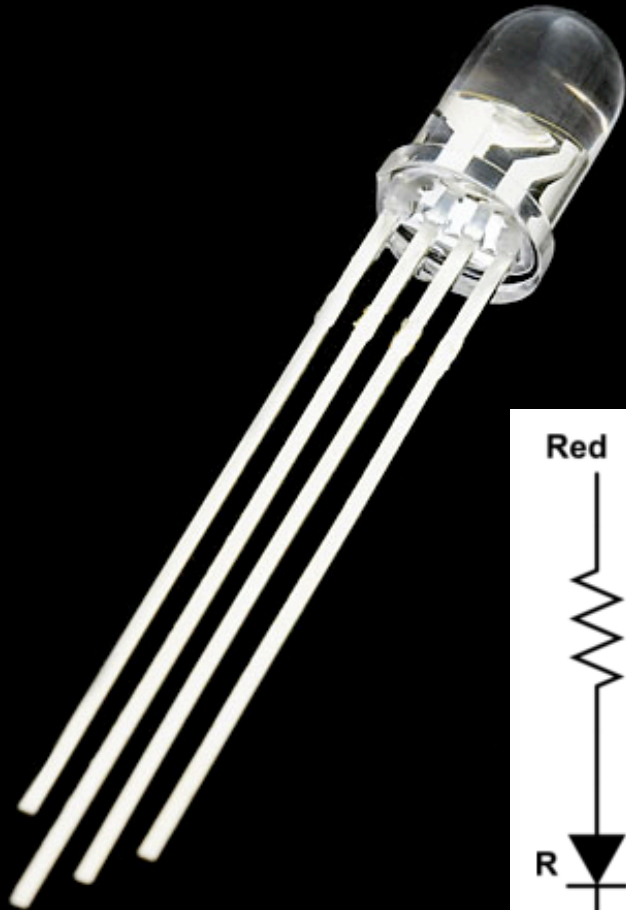

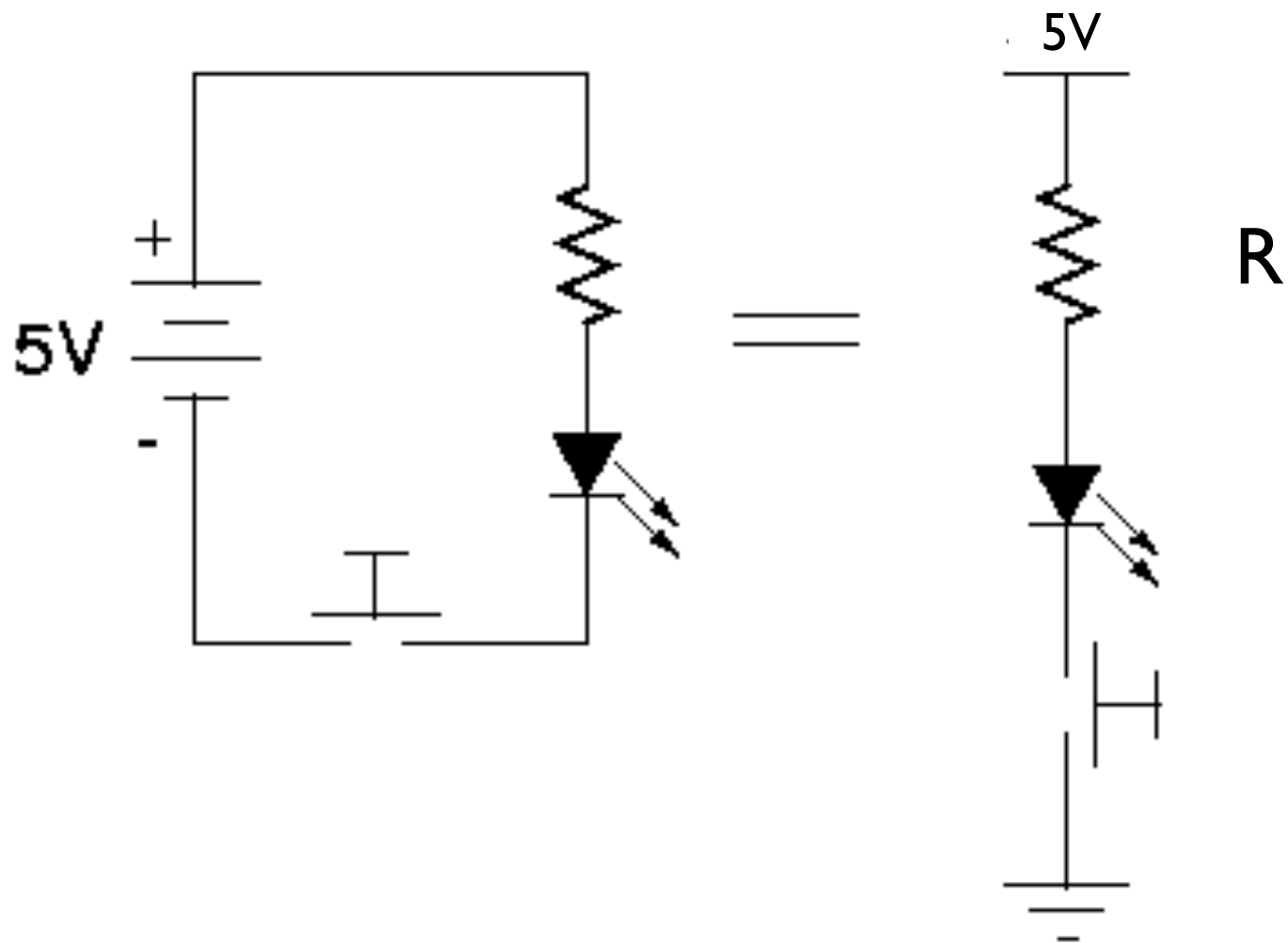Current regulation in the Pushbutton LED circuit



Ohm's Law states that Voltage = Current X Resistance


$$V=IR$$

Watt's Law states that Power = Voltage x Current

$$P=VI= I^2R$$


Ohm's Law states that Voltage = Current X Resistance

$$V=IR$$

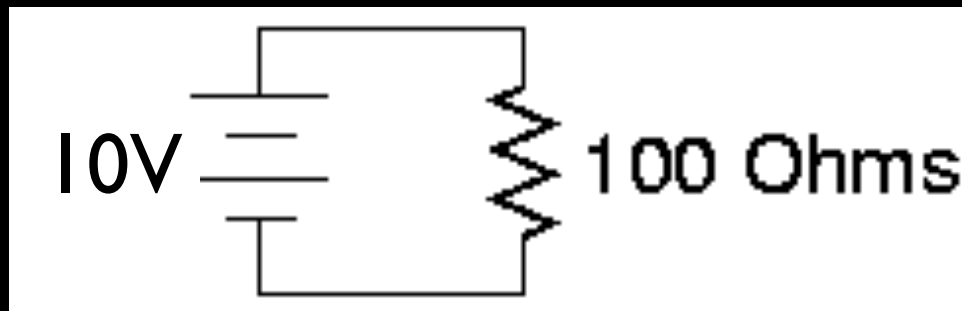


Ohm's Law states that Voltage = Current X Resistance

$$V=IR$$

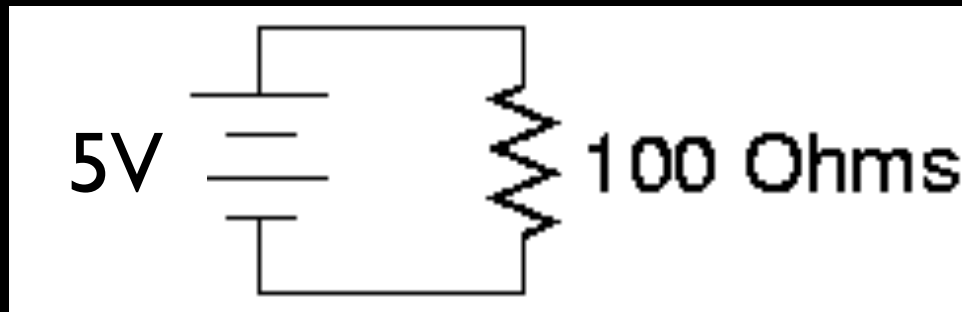

Equivalent Pushbutton LED circuit

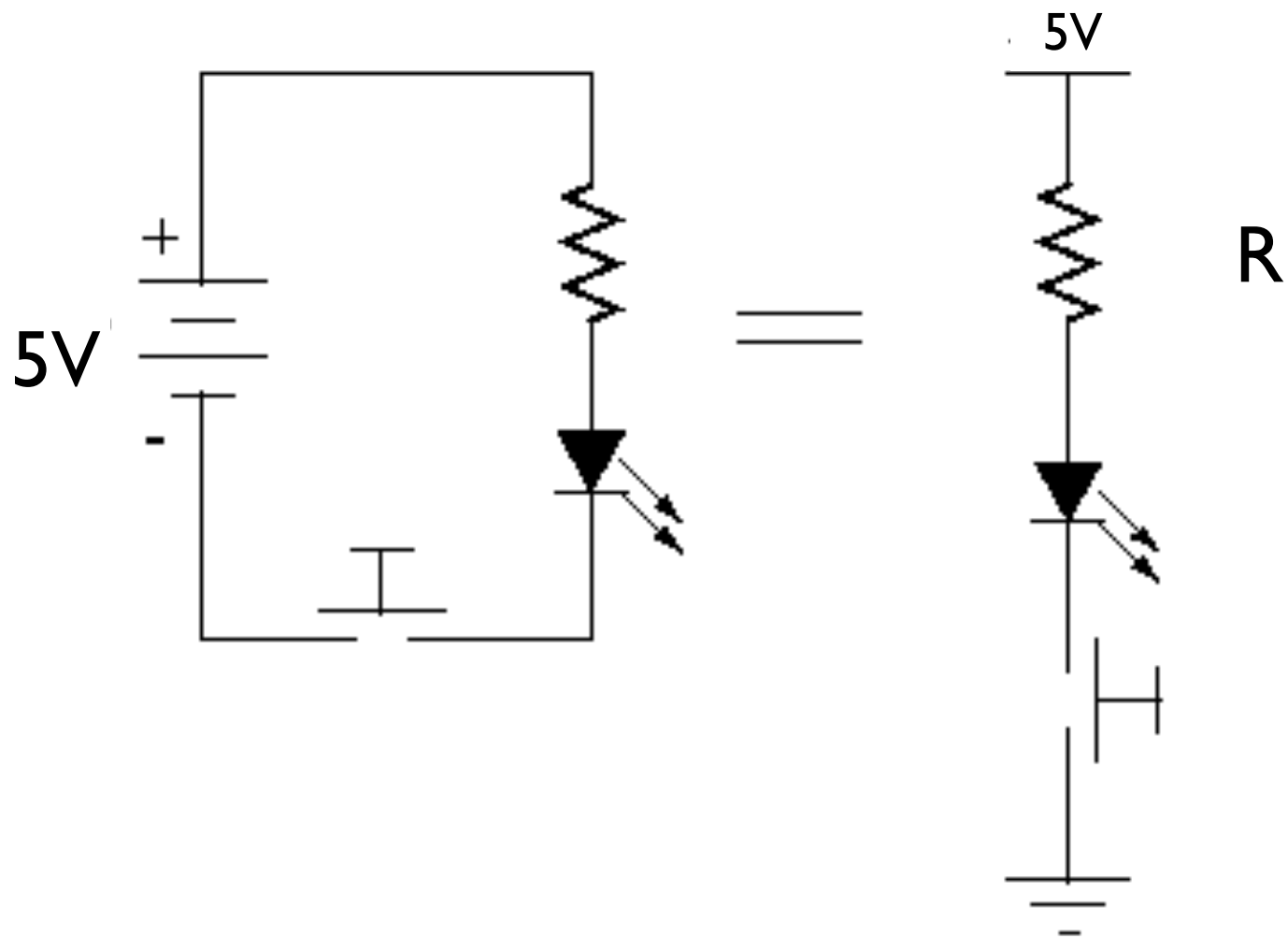

DON'T SHORT POWER TO GROUND


$$V=IR$$


$$I=V/R$$


$$\text{If } R=0, I = \infty$$

A little excitement

Why is this a **BAD** circuit?

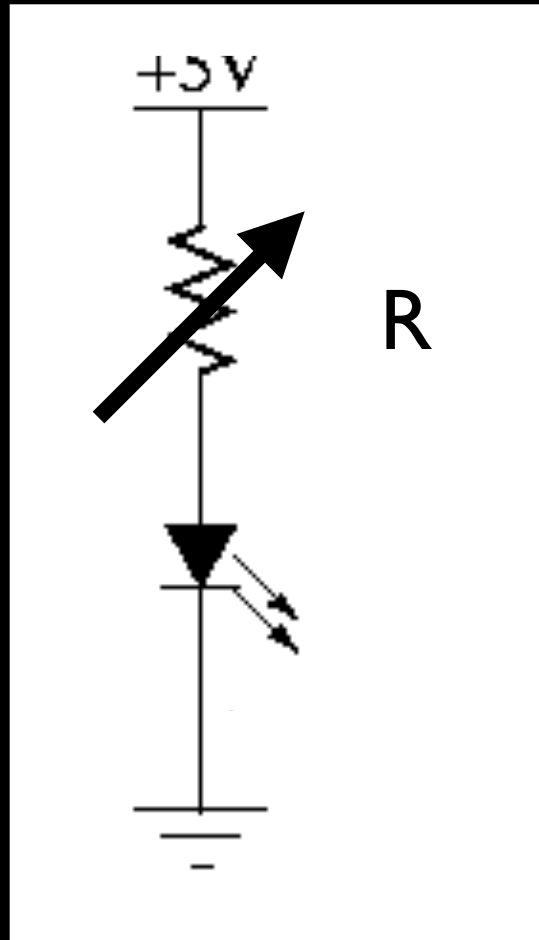


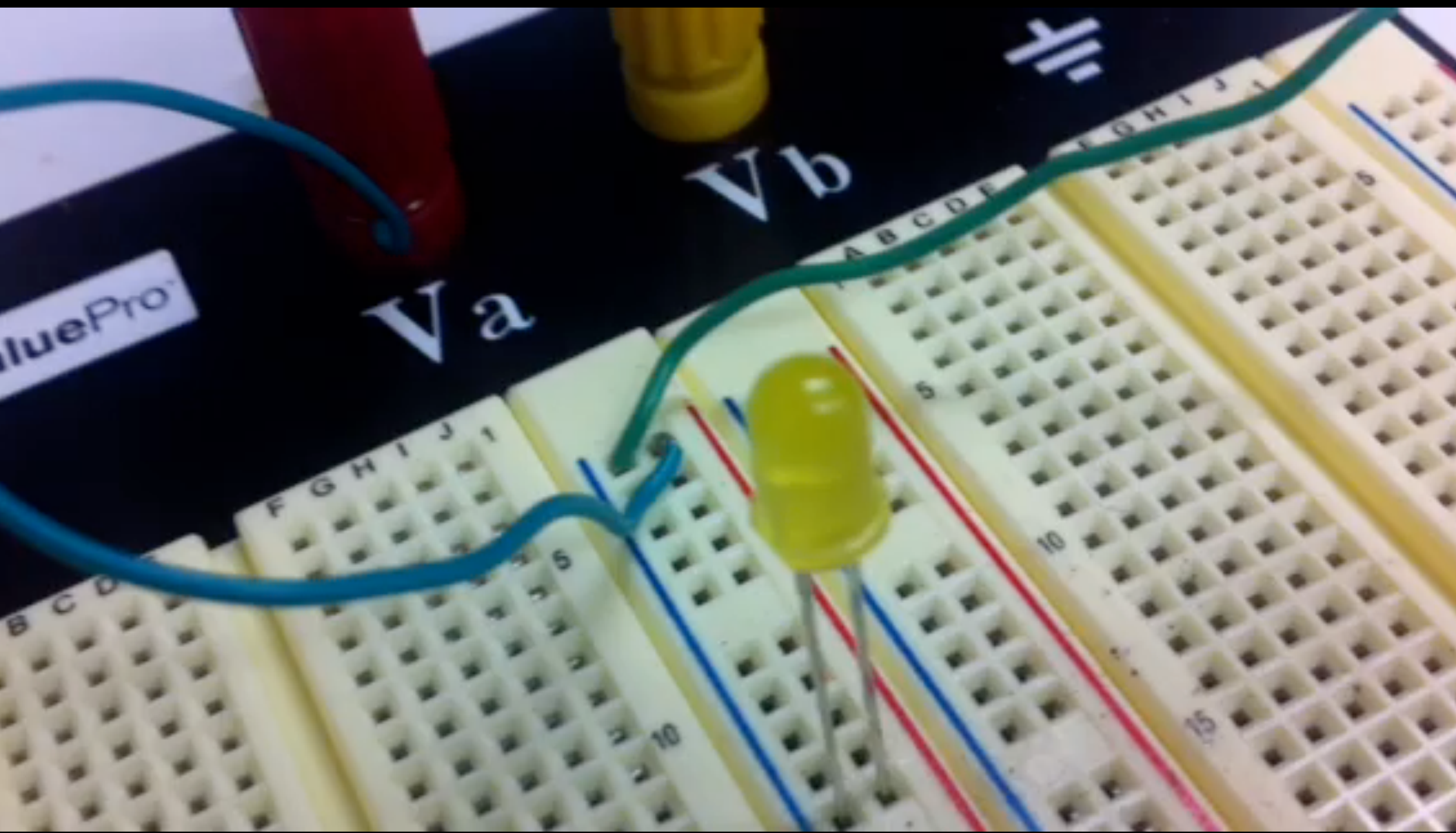

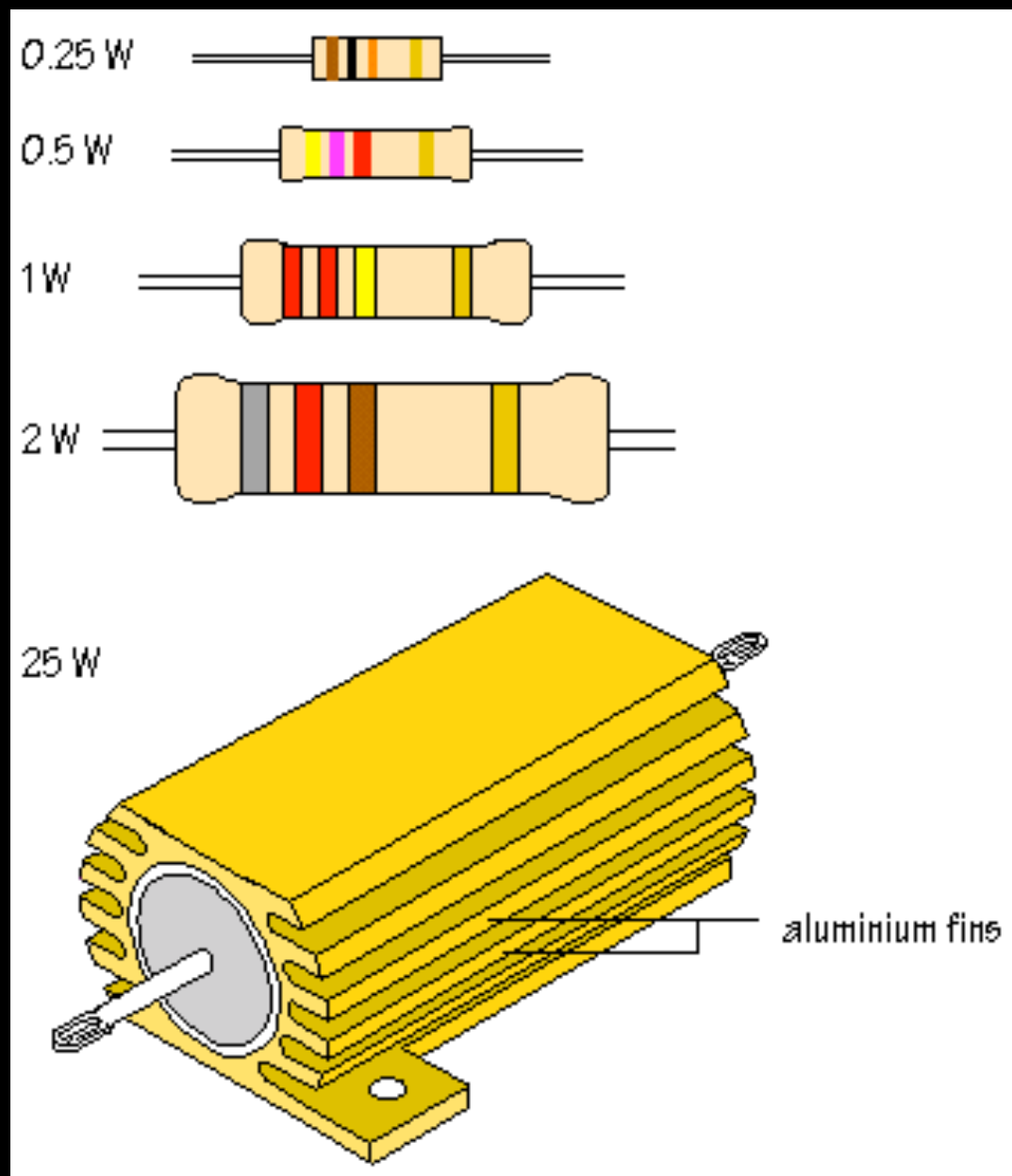


images from www.steiniche.dk/.../resistors-filer

READING RESISTANCE VALUES

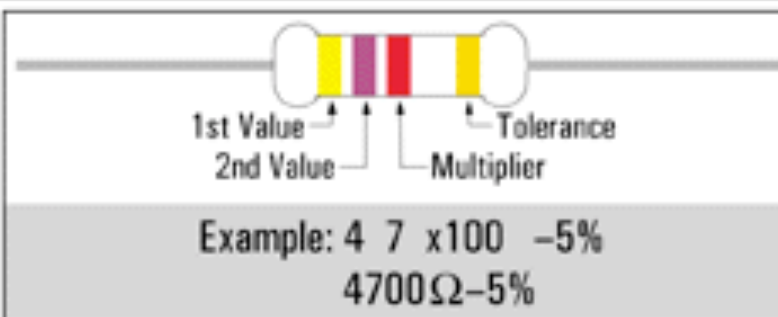


COLOR	VALUE	MULTIPLIER	TOLERANCE
Black	0	1	-
Brown	1	10	-1%
Red	2	100	-2%
Orange	3	1K	-
Yellow	4	10K	-
Green	5	100K	-.5%
Blue	6	1M	-.25%
Violet	7	10M	-.1%
Gray	8	100M	-.05%
White	9	1000M	-
Gold	-	1/10	-5%
Silver	-	1/100	-10%
None	-	-	-20%

Resistors in series **ADD**

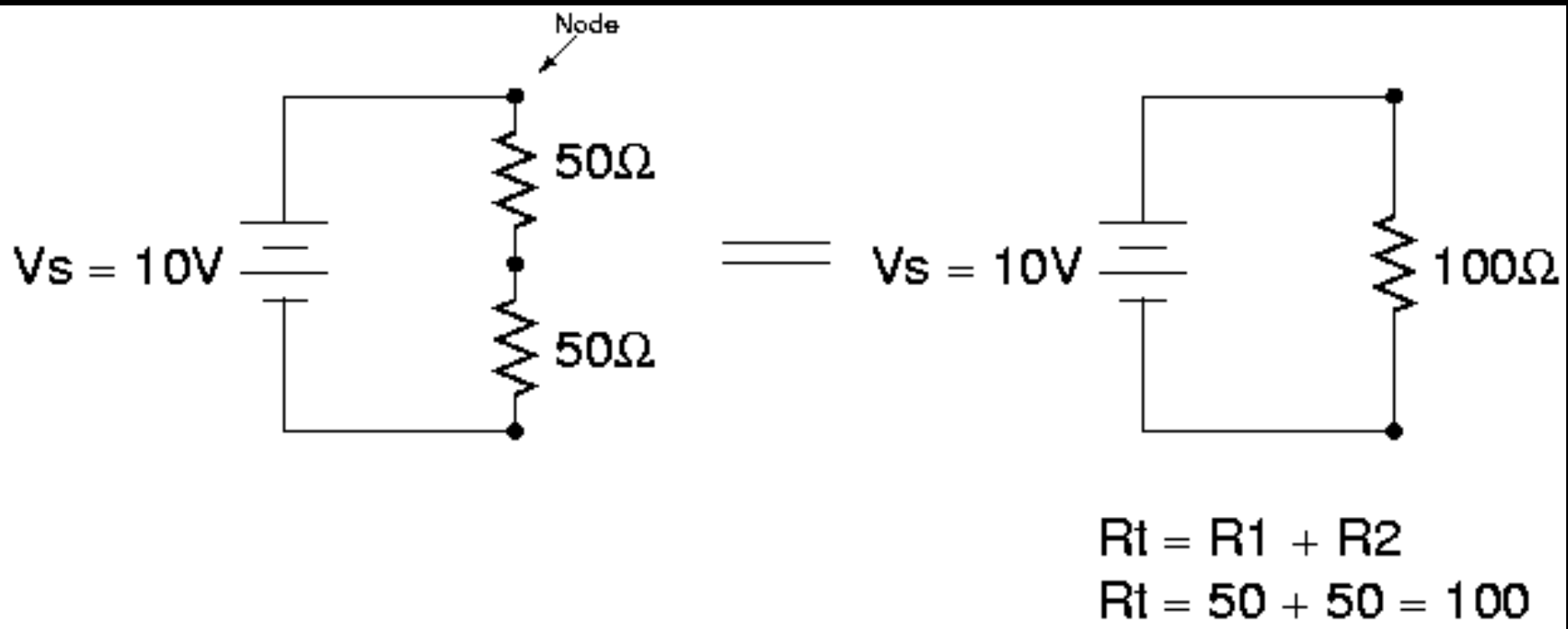


Resistors in parallel **DIVIDE**

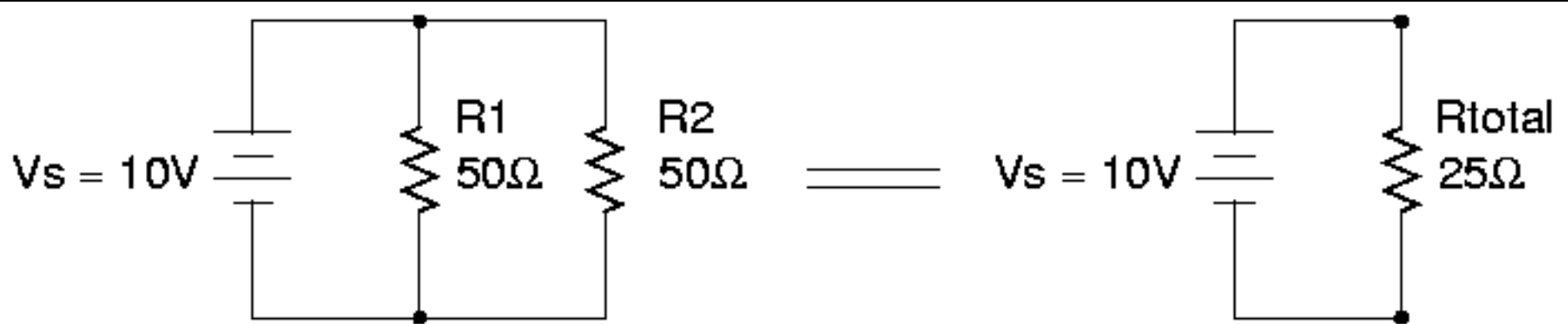

For Parallel Circuits:

$$R_{total} = (R_1 * R_2) / (R_1 + R_2)$$

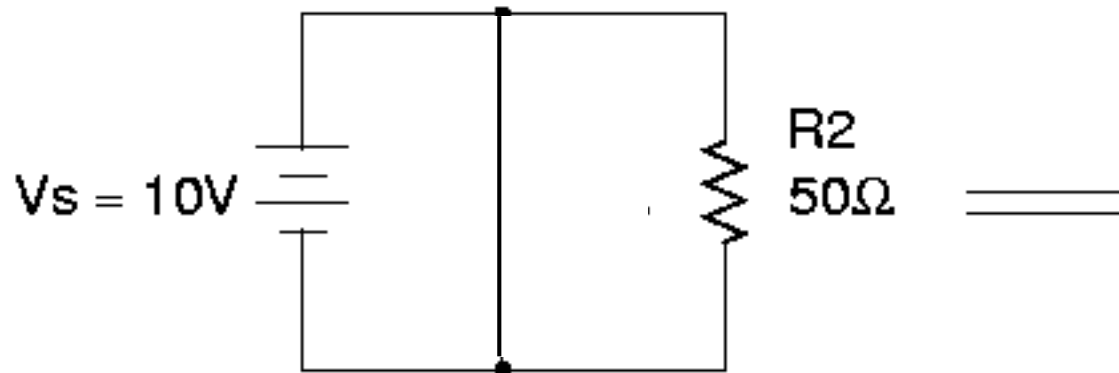
What is a **SHORT CIRCUIT**??? Why is this bad?




For Parallel Circuits:

$$R_{total} = (R_1 * R_2) / (R_1 + R_2)$$


VOLTAGE DIVIDER CIRCUIT

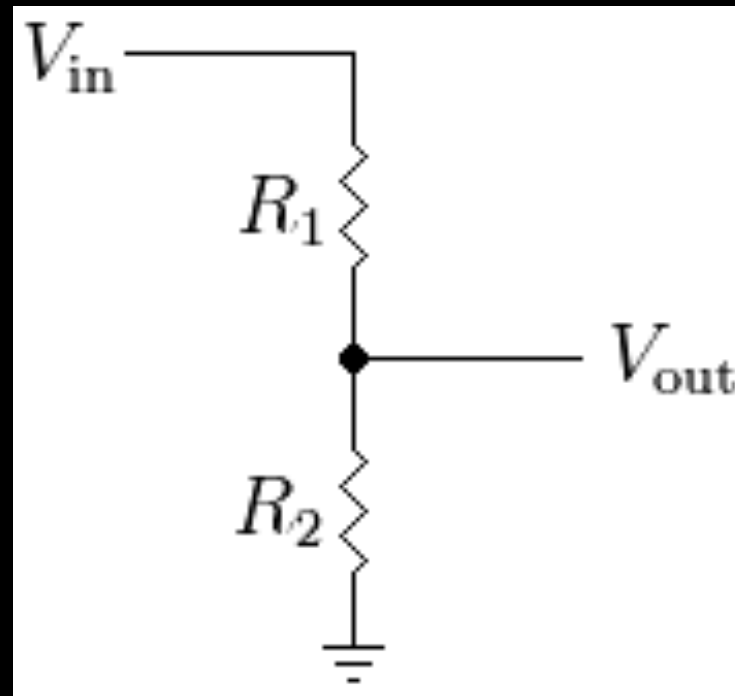

PULL UP RESISTOR


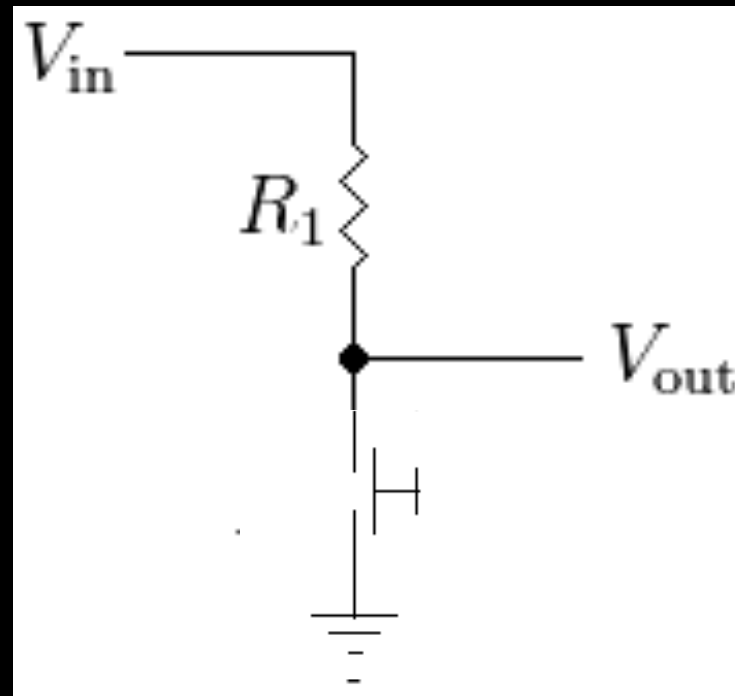


PULL DOWN RESISTOR

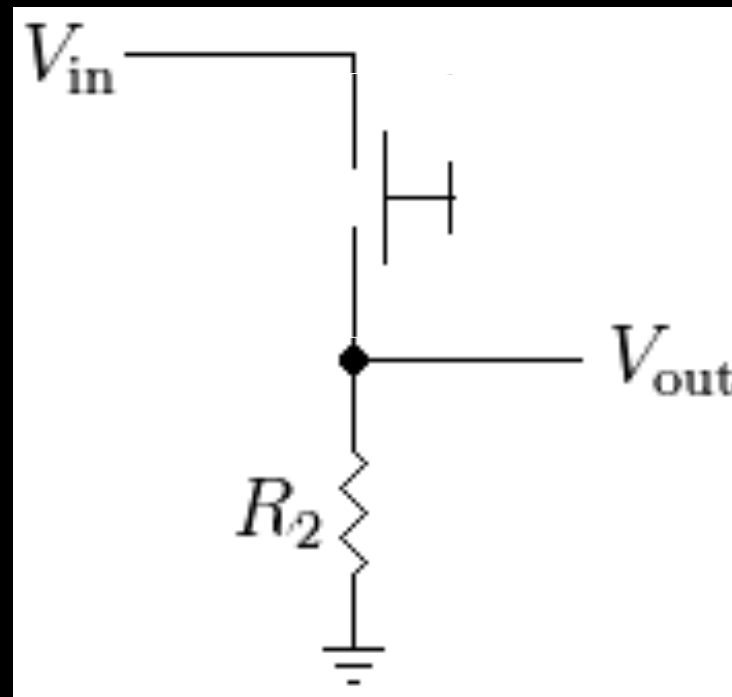


Adjusting the brightness of your LEDs

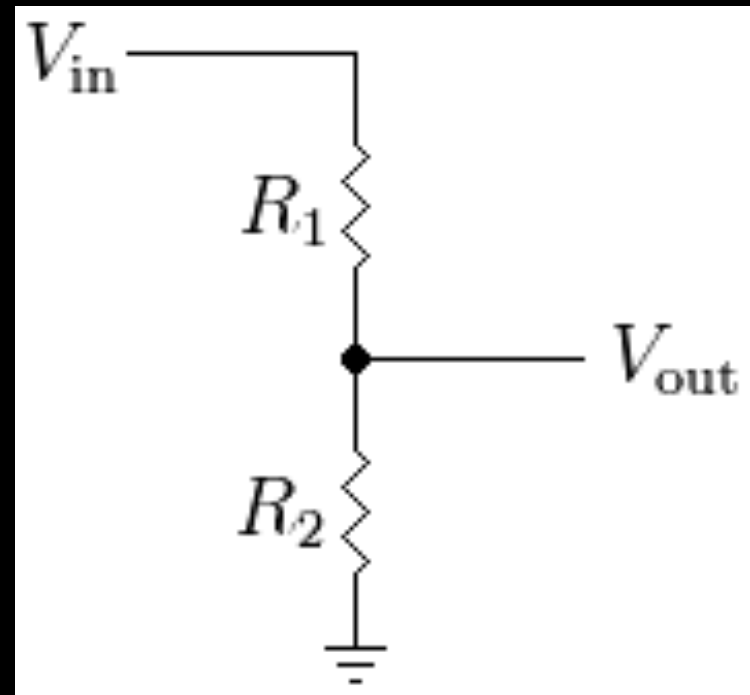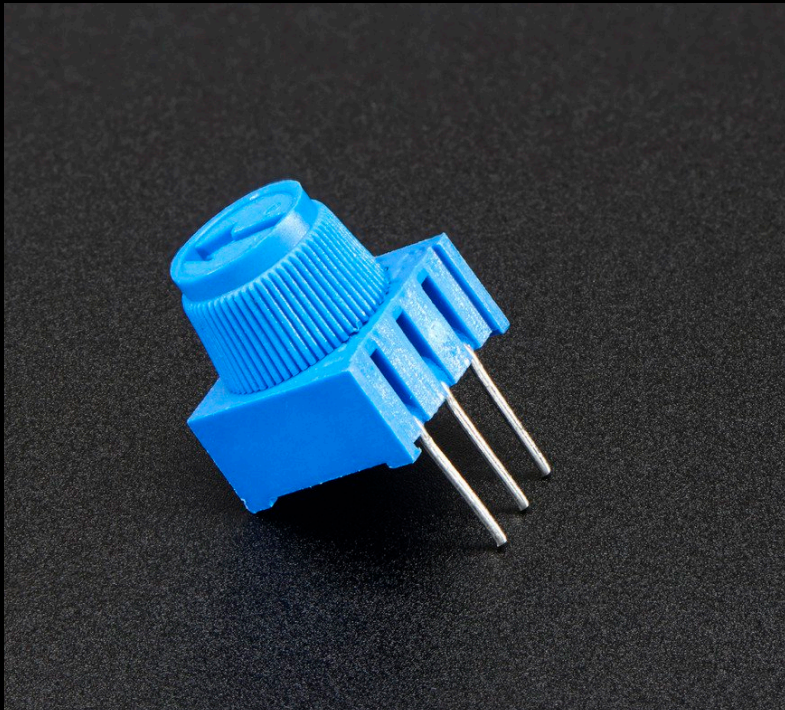A potentiometer is a variable resistor,
a voltage divider in a package.



Adjusting the brightness of your LEDs

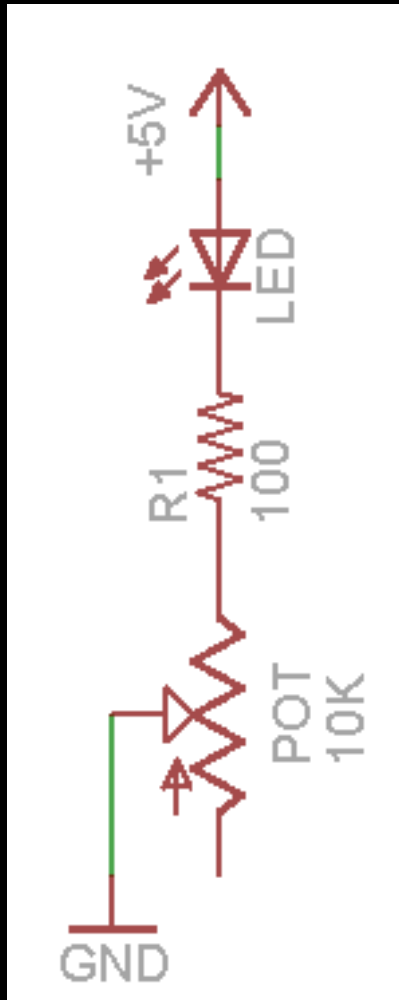


The **LED** is a diode, with a fixed voltage drop.


The **Current** is set by the series resistor

The brightness of the LED is a function of the current, created by the **resistance**.


$$I = V/R$$

Why is this a **BAD** circuit?

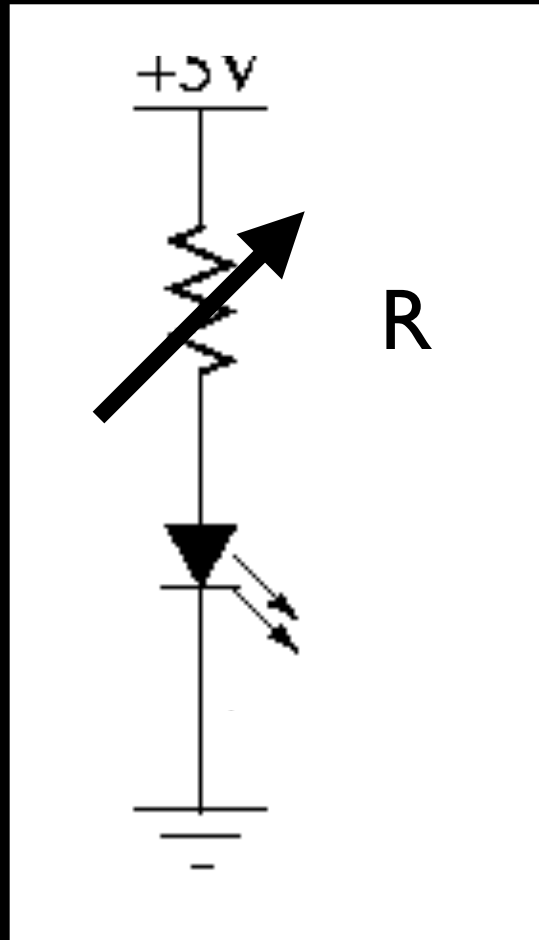

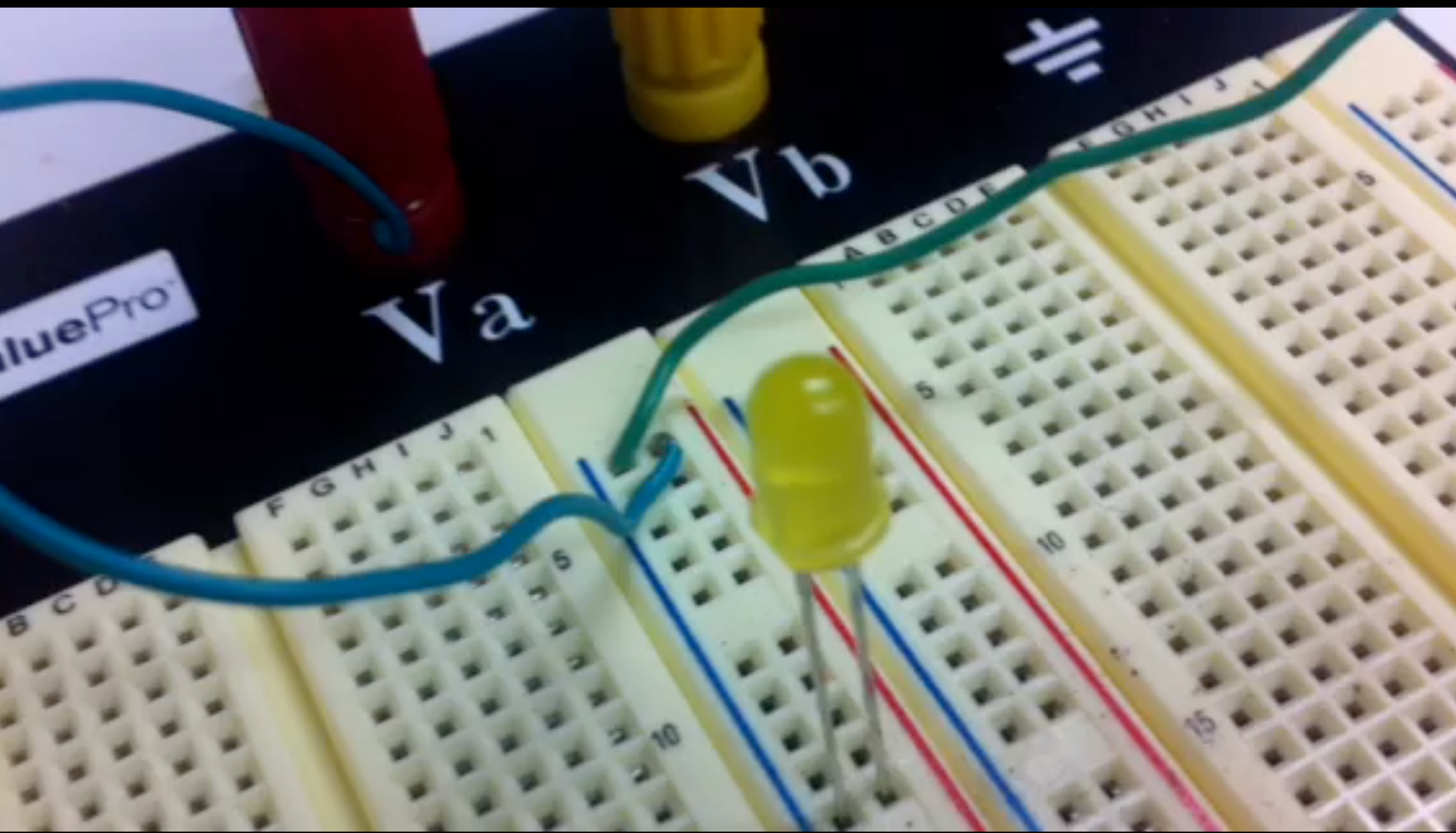

Pushbutton LED circuit

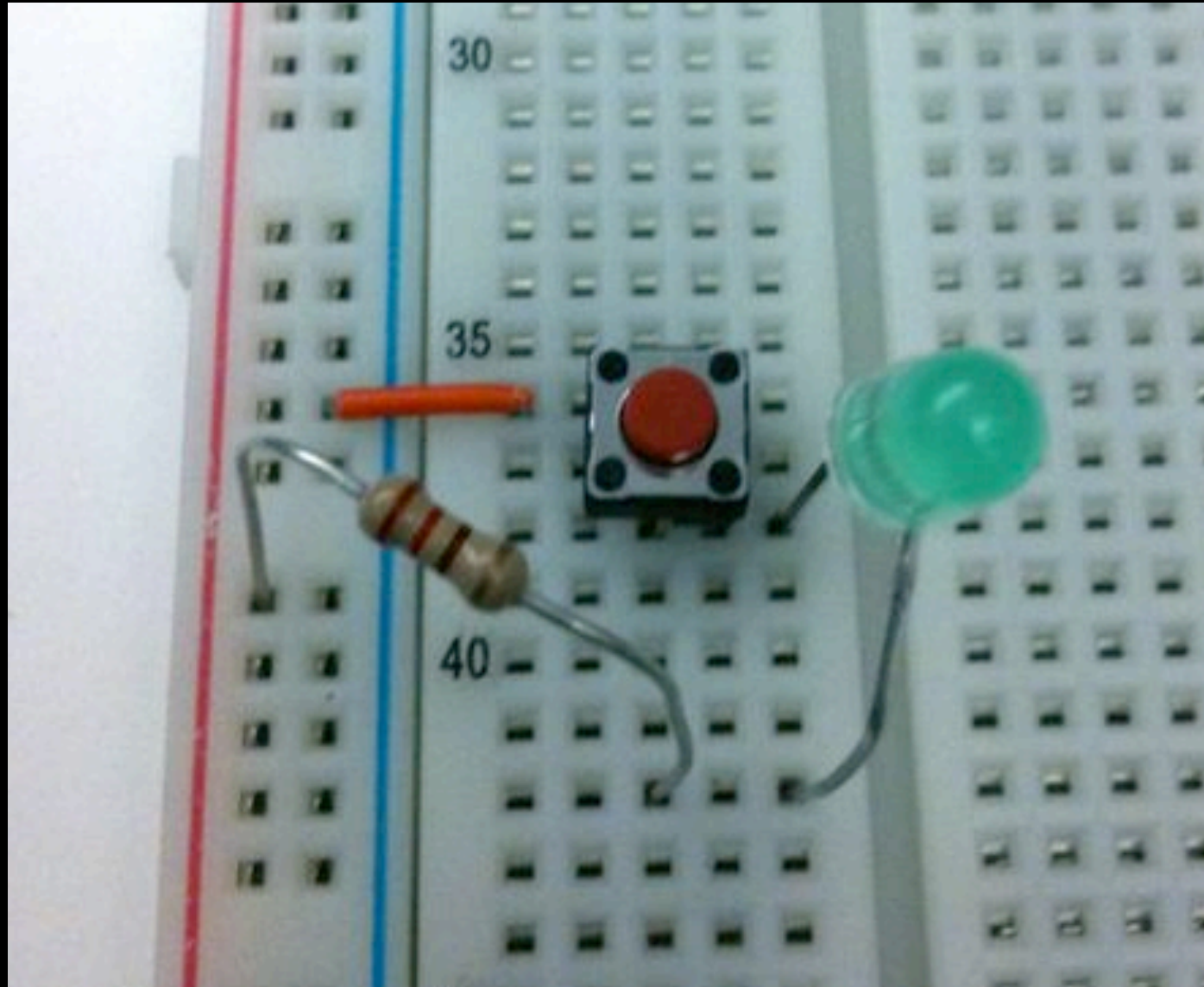

Pushbutton LED circuit breadboard drawing

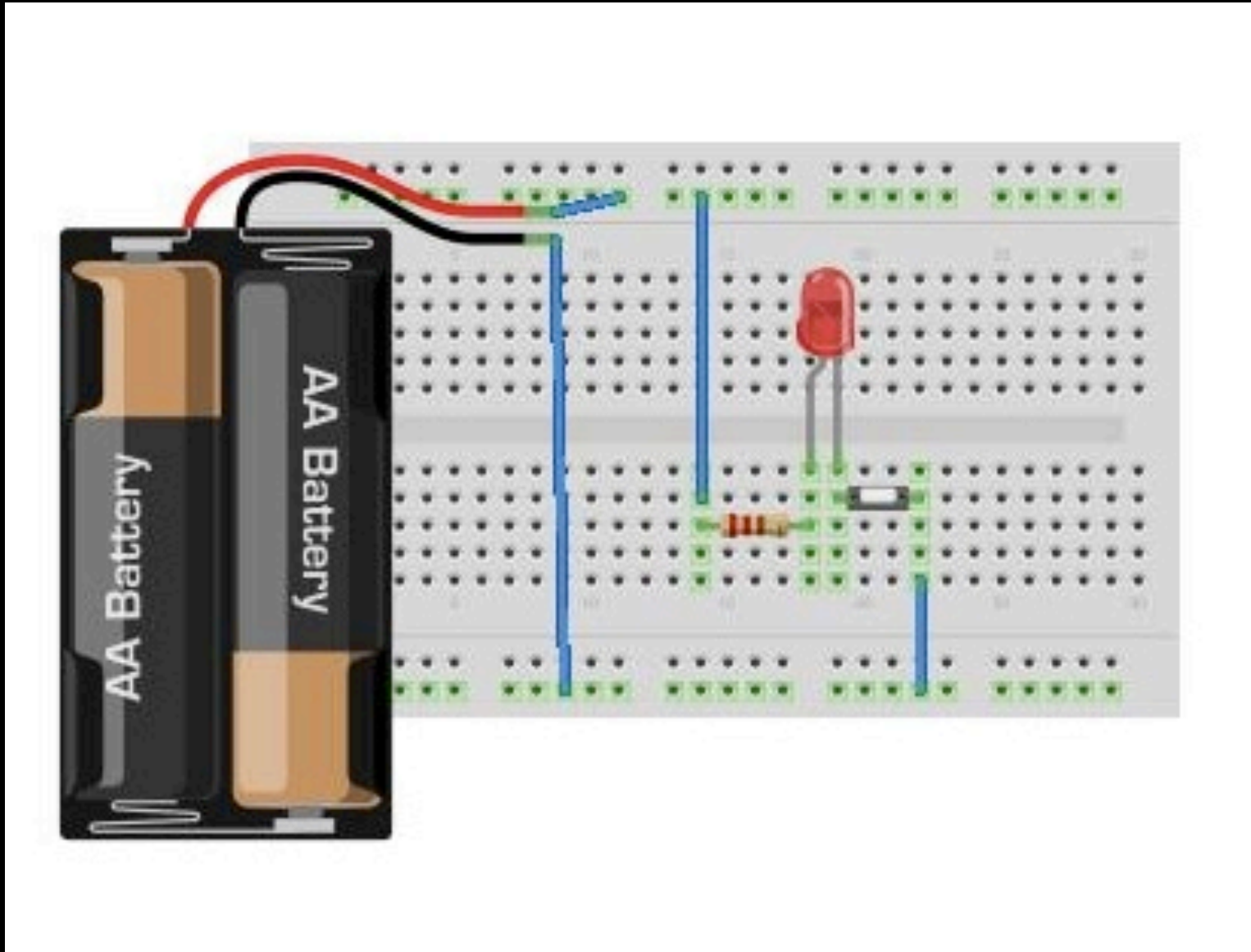


diagram made in Fritzing

Pushbutton LED circuit schematic

